



Power, Circuits & Schematics

Press Play: Interactive Device Design | March 30, 2011


Abstraction



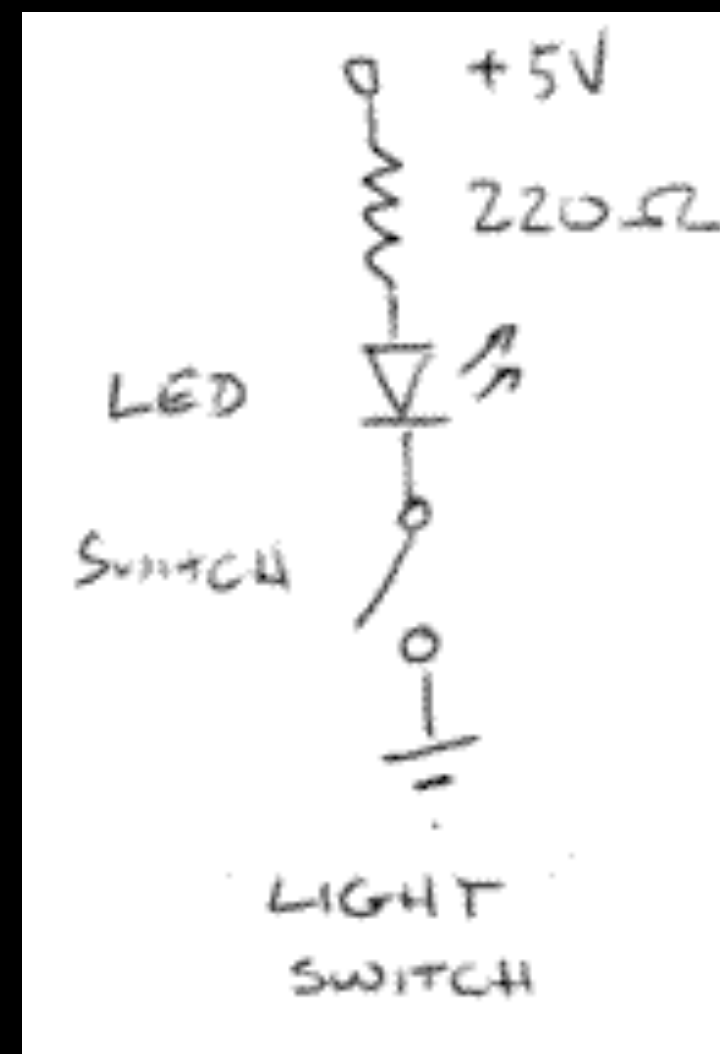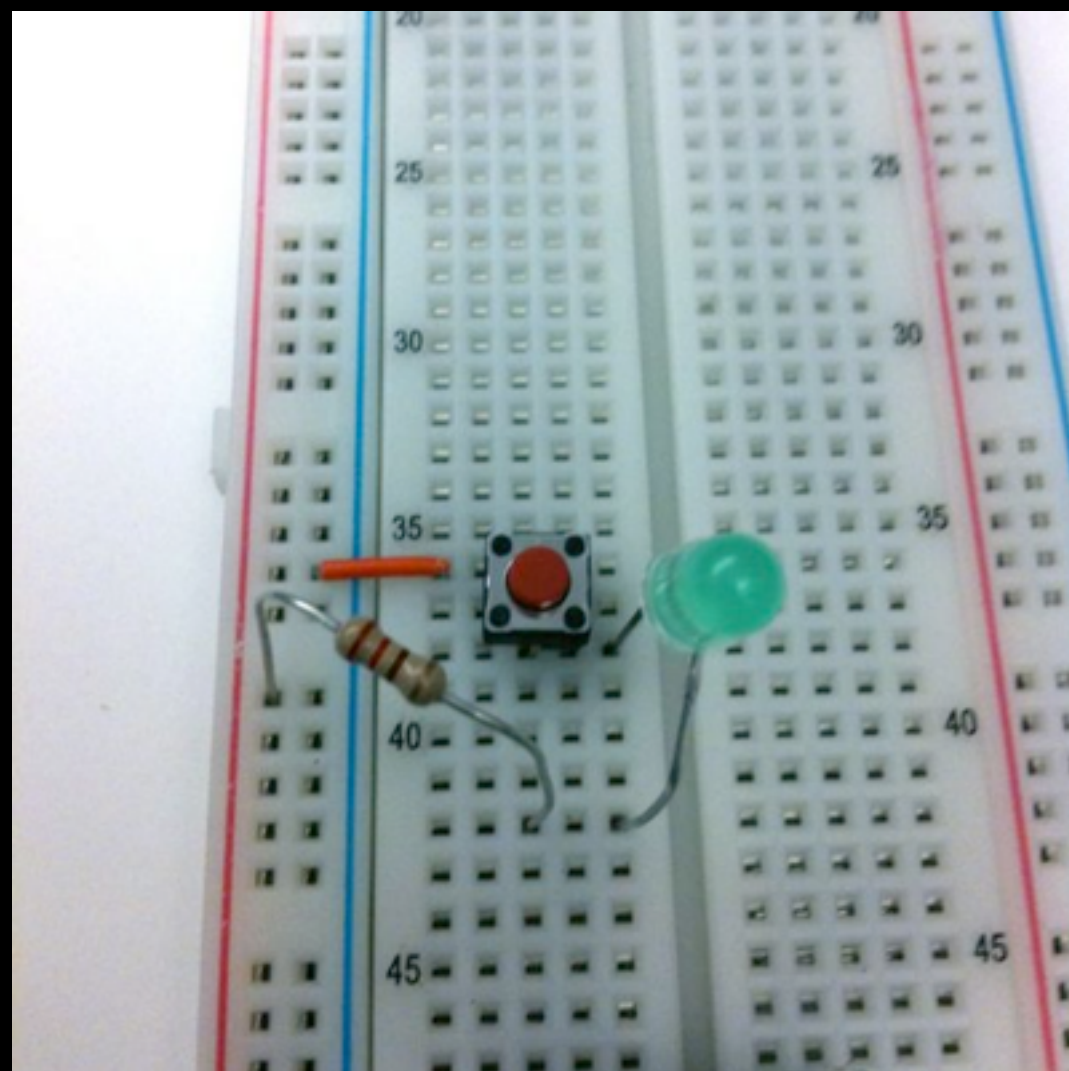images from solo2.abac.com/themole/geo_tubemap.gif



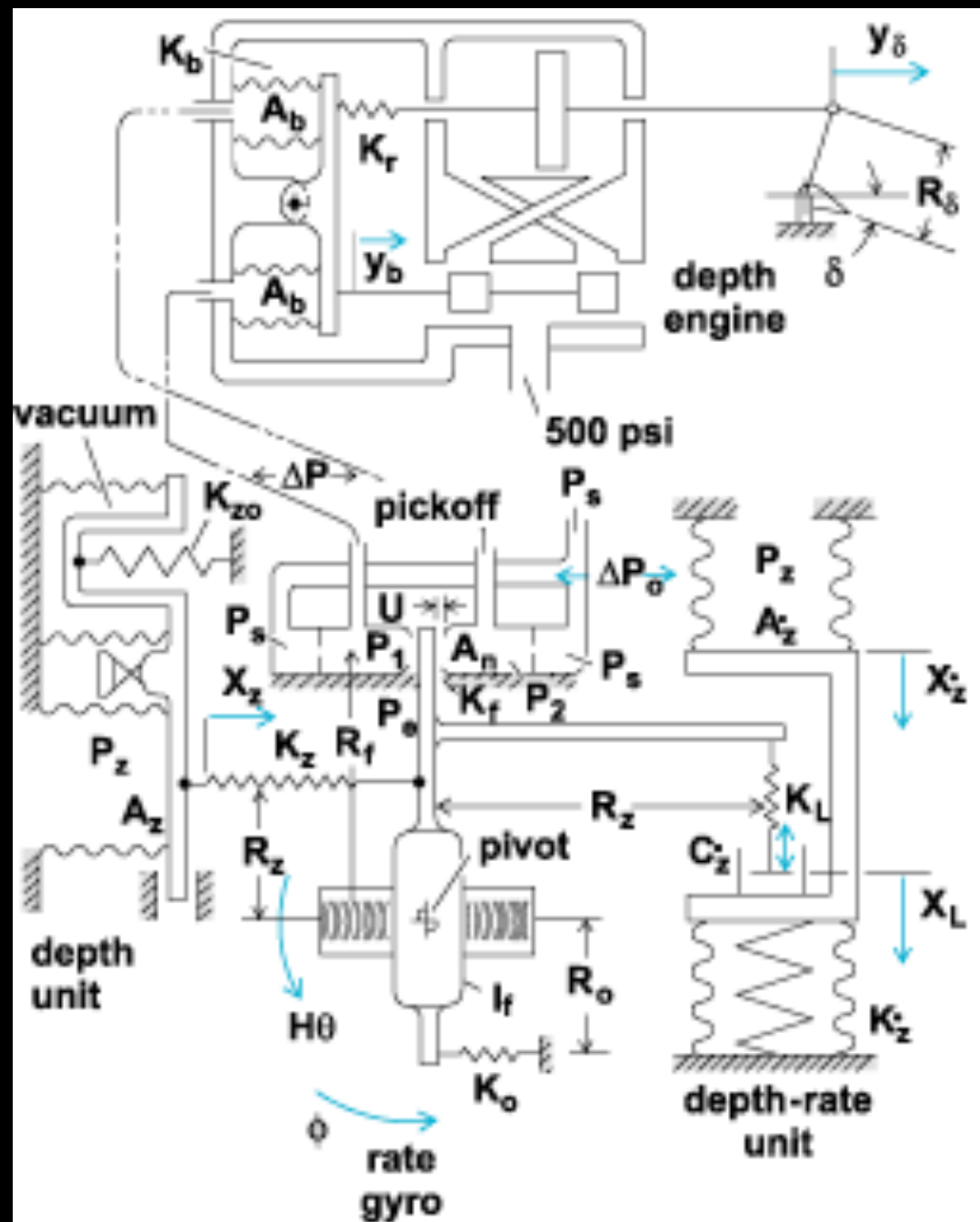images from <http://gizmolab.pbworks.com/Arduino-Tutorial-1%3A-Buttons-and-LEDs>



Subscripts:

b = differential-
pressure bellows

e = environment

f = flapper

L = depth-rate linkage

n = nozzles

o = ground, or reference

r = ram feedback

s = supply

z = depth unit

ż = depth-rate unit

δ = elevator

images from <http://www.answers.com/topic/schematic-diagram-graphic-arts>



images from www.sapdesignguild.org/

Circuits




Common Components | Voltage | Current | Resistance

Ohms Law | Watt's Law | Series and Parallel Circuits

Voltage Divider | Pull-up and Pull-down circuits

Electrical circuits are networks of electrical elements that contain a closed loop which allows electrons to flow through the elements.

Examples of Electrical Components

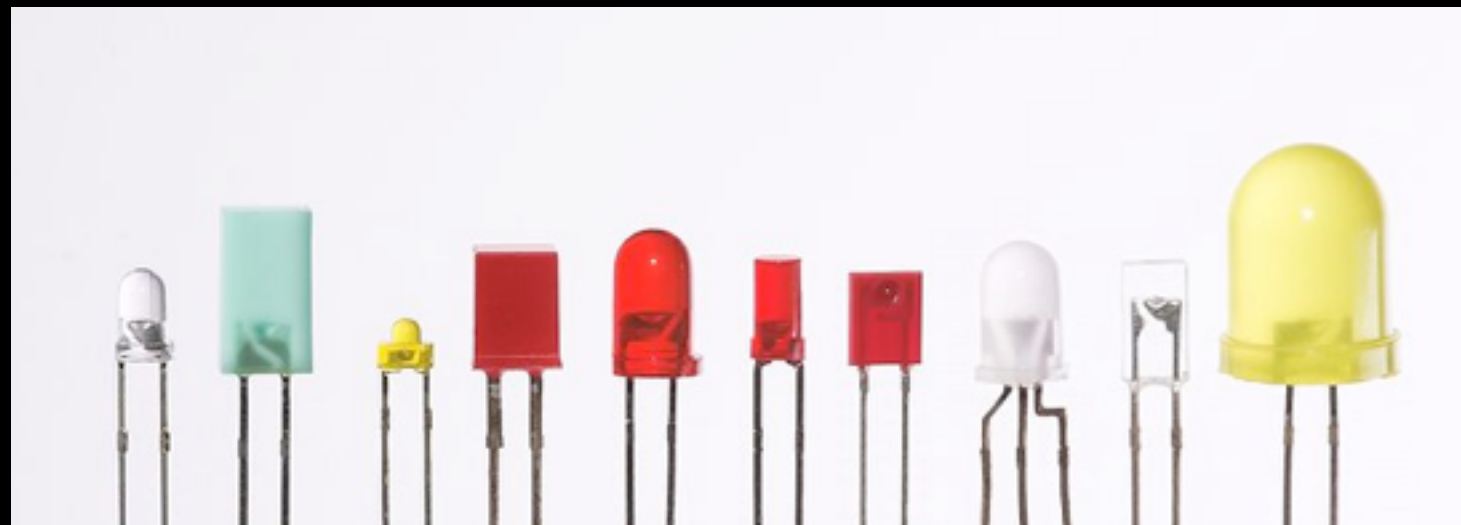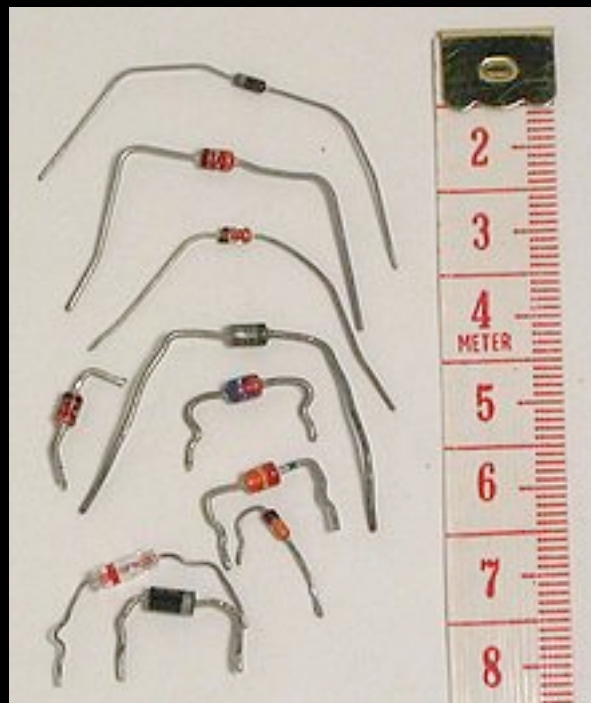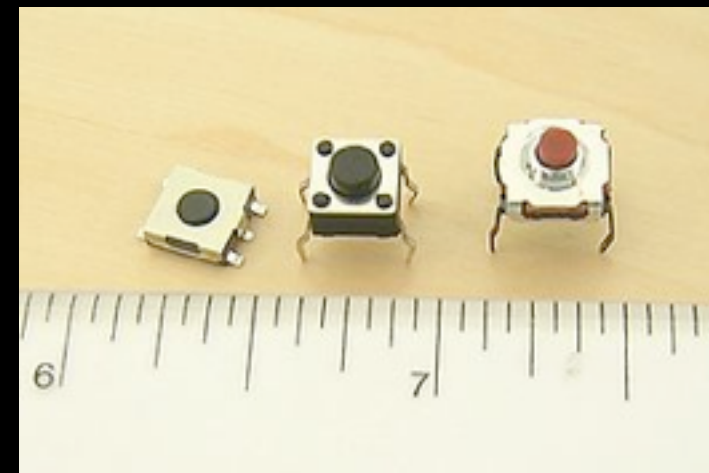

images from Wikipedia


Current (measured in Amperes or Amps) is the quantity of electrons passing through a point in a circuit.

Voltage (measured in Volts) is the potential difference in electrical charge between two points in a circuit.


Resistance (measured in Ohms) is the capacity of a circuit element to impede the flow of electrons in an electrical circuit.

Ohm's Law states that Voltage = Current X Resistance


$$V=IR$$

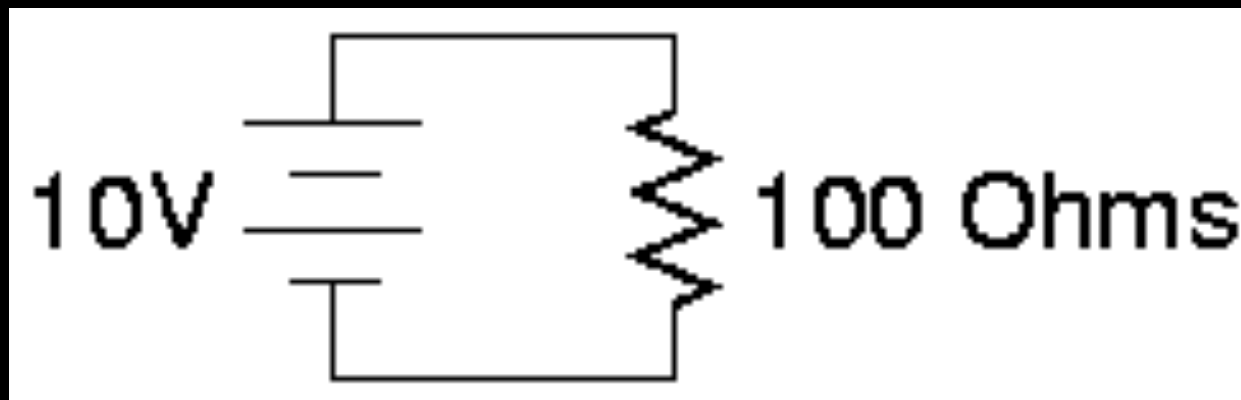

Example: Button LED circuit

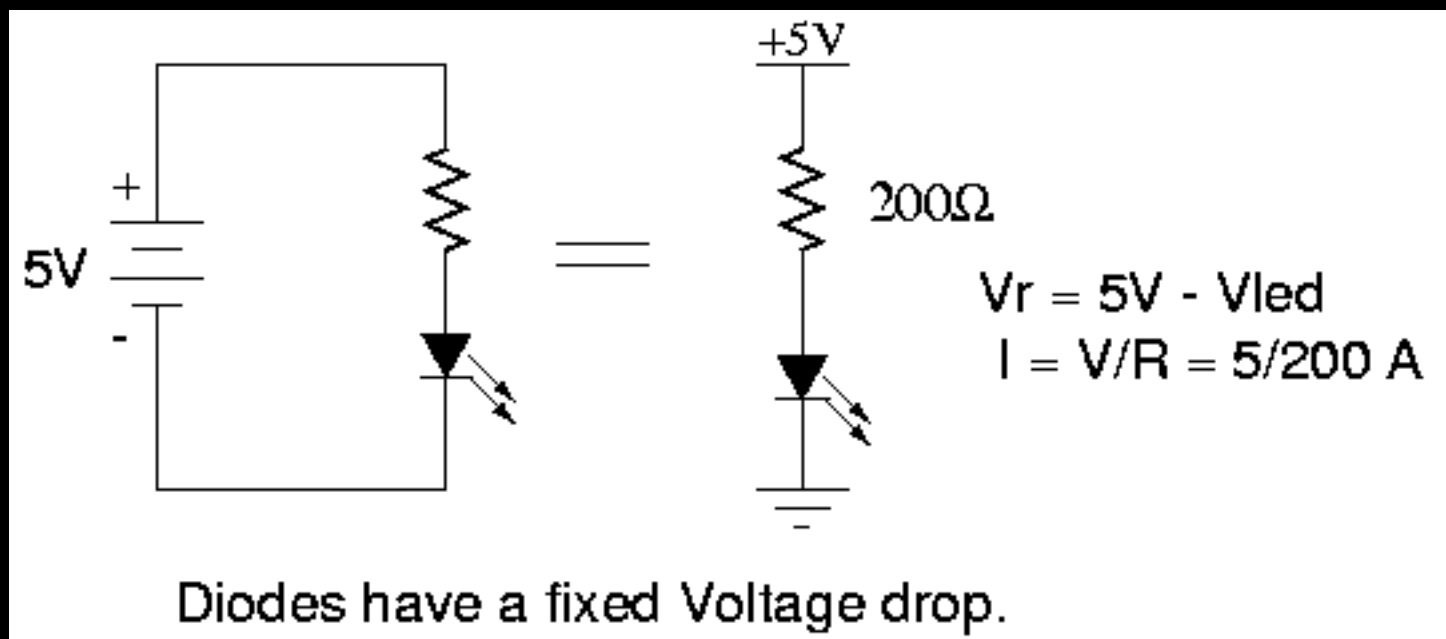


Example: Button LED circuit

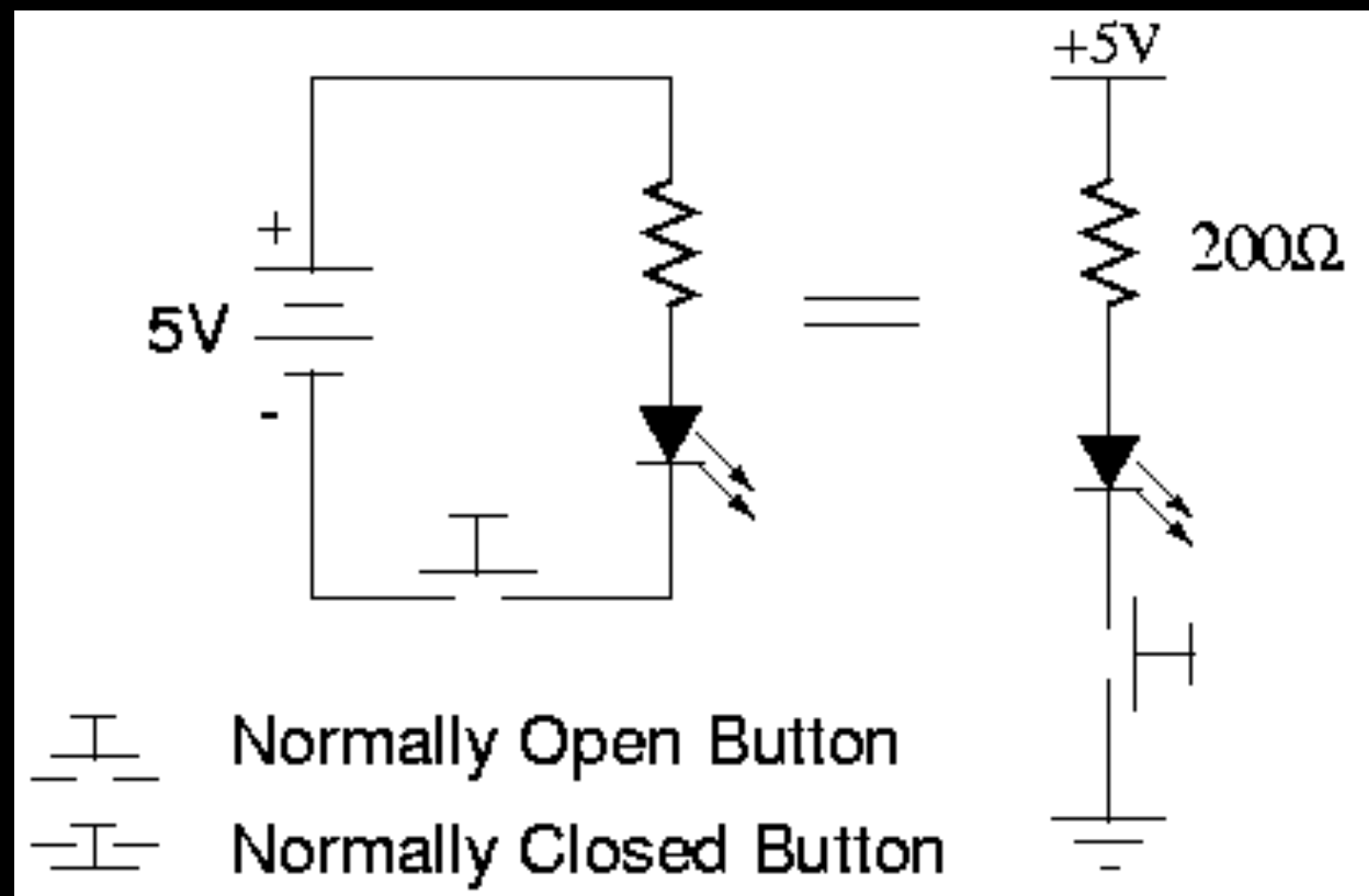


Watt's Law states that Power = Voltage x Current

$$P=VI= I^2R$$

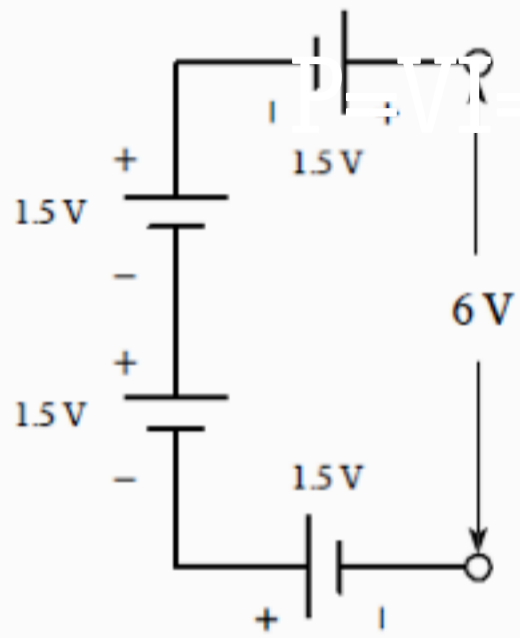
Power can come from supplies or batteries.



Increasing the voltage





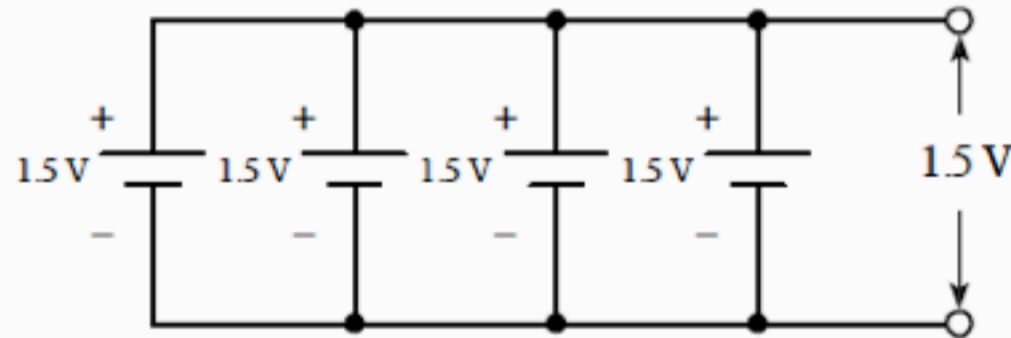


Increasing the capacity

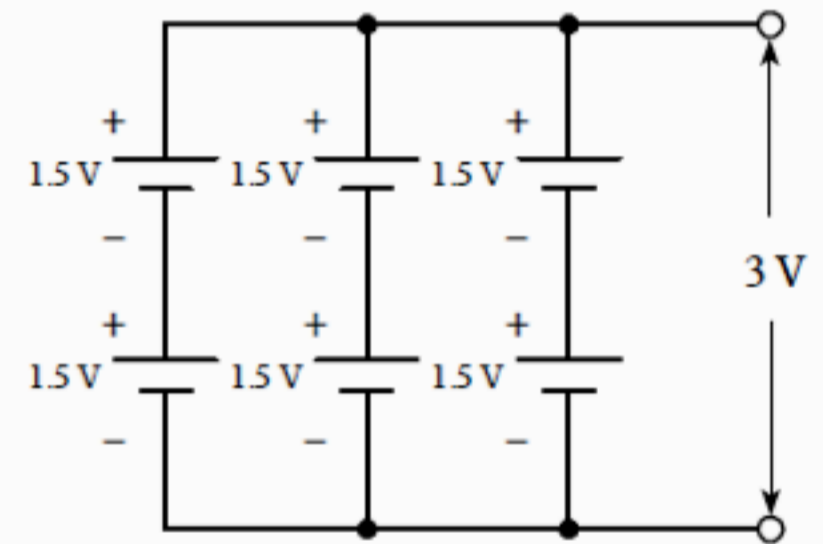

Increasing both voltage and capacity

Common Alkaline and Carbon Zinc Cells

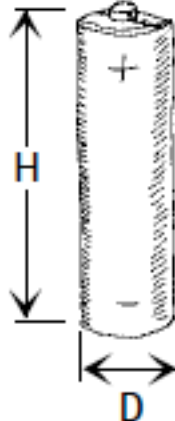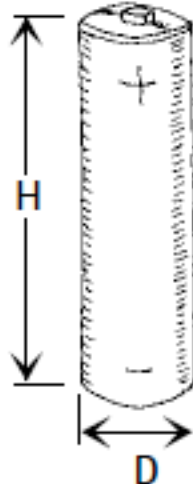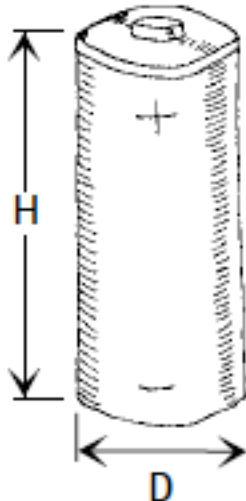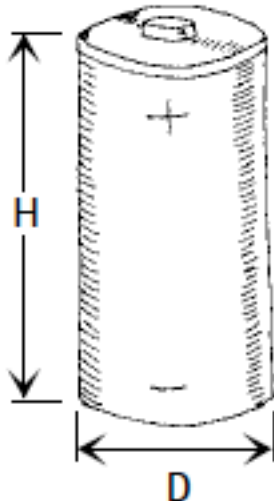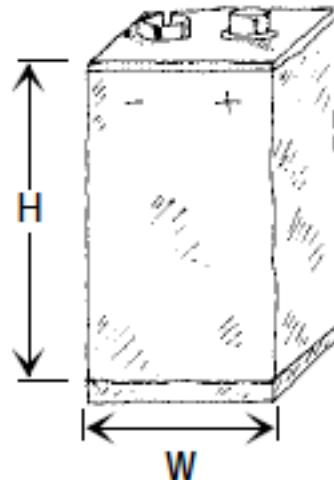1.5V "AAA"	1.5V "AA"	1.5V "C"	1.5V "D"	"9V"																																	
																																					
<table><tr><th>D</th><th>H</th></tr><tr><td>0.41"</td><td>1.75"</td></tr><tr><td>$\left(\frac{13}{32}\right)$</td><td>$\left(1\frac{31}{32}\right)$</td></tr></table>	D	H	0.41"	1.75"	$\left(\frac{13}{32}\right)$	$\left(1\frac{31}{32}\right)$	<table><tr><th>D</th><th>H</th></tr><tr><td>0.56"</td><td>1.97"</td></tr><tr><td>$\left(\frac{9}{16}\right)$</td><td>$\left(1\frac{31}{32}\right)$</td></tr></table>	D	H	0.56"	1.97"	$\left(\frac{9}{16}\right)$	$\left(1\frac{31}{32}\right)$	<table><tr><th>D</th><th>H</th></tr><tr><td>1.02"</td><td>1.97"</td></tr><tr><td>$\left(1\frac{1}{64}\right)$</td><td>$\left(1\frac{31}{32}\right)$</td></tr></table>	D	H	1.02"	1.97"	$\left(1\frac{1}{64}\right)$	$\left(1\frac{31}{32}\right)$	<table><tr><th>D</th><th>H</th></tr><tr><td>1.32"</td><td>2.39"</td></tr><tr><td>$\left(\frac{11}{32}\right)$</td><td>$\left(2\frac{27}{64}\right)$</td></tr></table>	D	H	1.32"	2.39"	$\left(\frac{11}{32}\right)$	$\left(2\frac{27}{64}\right)$	<table><tr><th>W</th><th>L</th><th>H</th></tr><tr><td>1.03"</td><td>0.65"</td><td>1.91"</td></tr><tr><td>$\left(\frac{13}{32}\right)$</td><td>$\left(\frac{11}{16}\right)$</td><td>$\left(1\frac{15}{16}\right)$</td></tr></table>	W	L	H	1.03"	0.65"	1.91"	$\left(\frac{13}{32}\right)$	$\left(\frac{11}{16}\right)$	$\left(1\frac{15}{16}\right)$
D	H																																				
0.41"	1.75"																																				
$\left(\frac{13}{32}\right)$	$\left(1\frac{31}{32}\right)$																																				
D	H																																				
0.56"	1.97"																																				
$\left(\frac{9}{16}\right)$	$\left(1\frac{31}{32}\right)$																																				
D	H																																				
1.02"	1.97"																																				
$\left(1\frac{1}{64}\right)$	$\left(1\frac{31}{32}\right)$																																				
D	H																																				
1.32"	2.39"																																				
$\left(\frac{11}{32}\right)$	$\left(2\frac{27}{64}\right)$																																				
W	L	H																																			
1.03"	0.65"	1.91"																																			
$\left(\frac{13}{32}\right)$	$\left(\frac{11}{16}\right)$	$\left(1\frac{15}{16}\right)$																																			

Lithium



Voltage:
 1.55 to 6V
 Diameter:
 0.460 to 0.965"
 Thicknesses:
 0.079" to 0.990"
 mAh:
 60 to 250 mAh
 Label:
 Given in I.E.C.
 number (e.g.,
 CRXXXX or BRXXXX)

Zinc air



Voltage:
 1.15 to 1.4V
 mAh:
 70 to 600 mAh
 Labels:
 ZAXXX

Mercury



Voltage:
 1.35 to 5.6V
 Diameter:
 0.5 to 0.695"
 Thicknesses:
 0.135" to 0.845"
 mAh:
 80 to 1000 mAh


Silver oxide



Voltage:
 1.55V
 Diameter:
 0.267 to 0.610"
 Thicknesses:
 0.81" to 0.210"
 mAh:
 15 to 250 mAh
 Label:
 Given in I.E.C.
 number (e.g., SRXX)


5V DC to DC Step Up - 1xAA



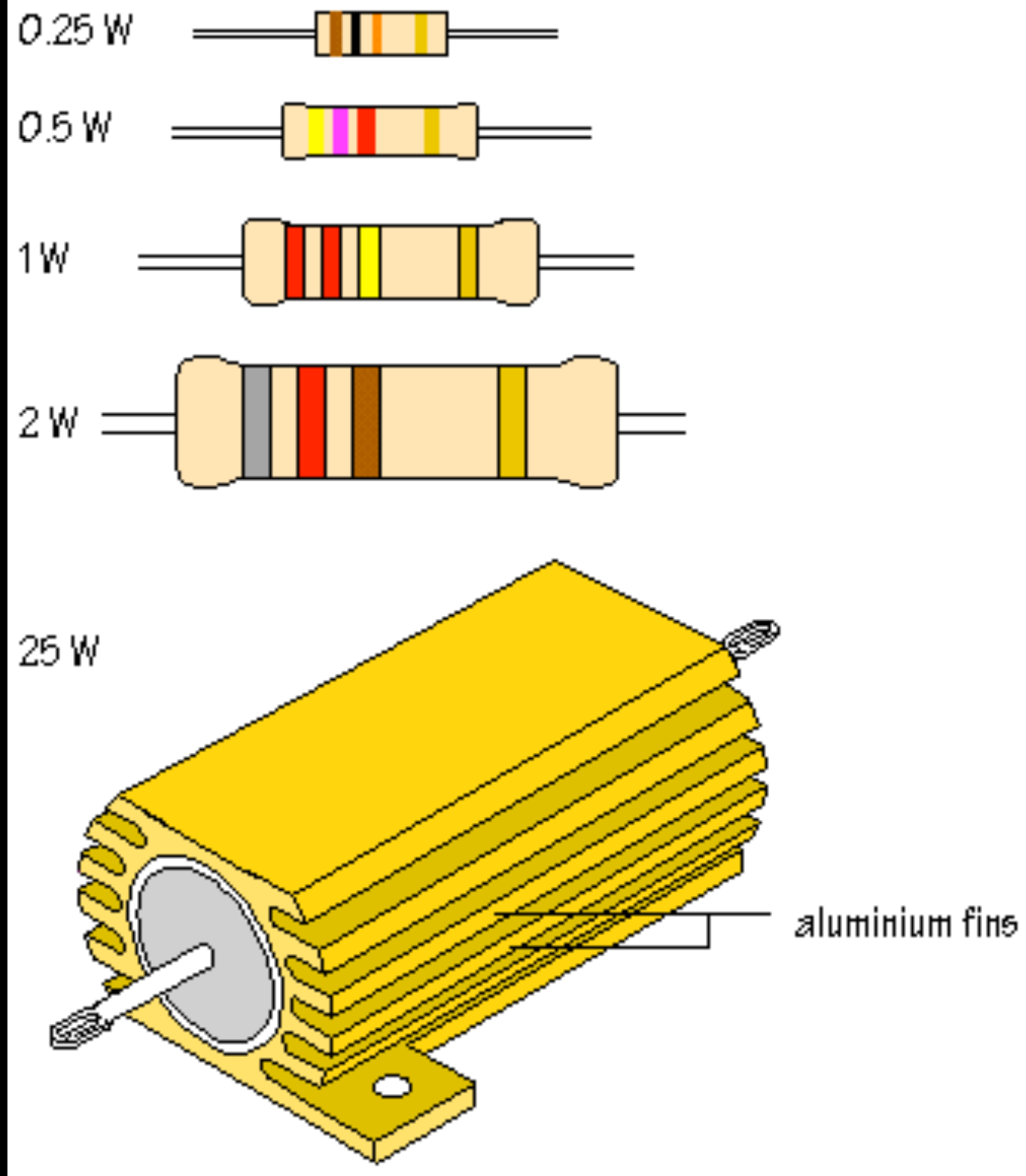


images from www.steiniche.dk/.../resistors-filer


READING RESISTANCE VALUES

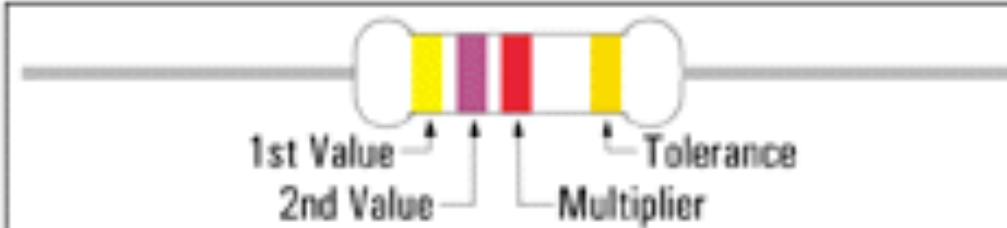

Example: 4 7 x100 -5%
4700Ω-5%

COLOR		VALUE	MULTIPLIER	TOLERANCE
Black		0	1	.
Brown		1	10	-1%
Red		2	100	-2%
Orange		3	1K	.
Yellow		4	10K	.
Green		5	100K	-.5%
Blue		6	1M	-.25%
Violet		7	10M	-.1%
Gray		8	100M	-.05%
White		9	1000M	.
Gold		.	1/10	-5%
Silver		.	1/100	-10%
None		.	.	-20%

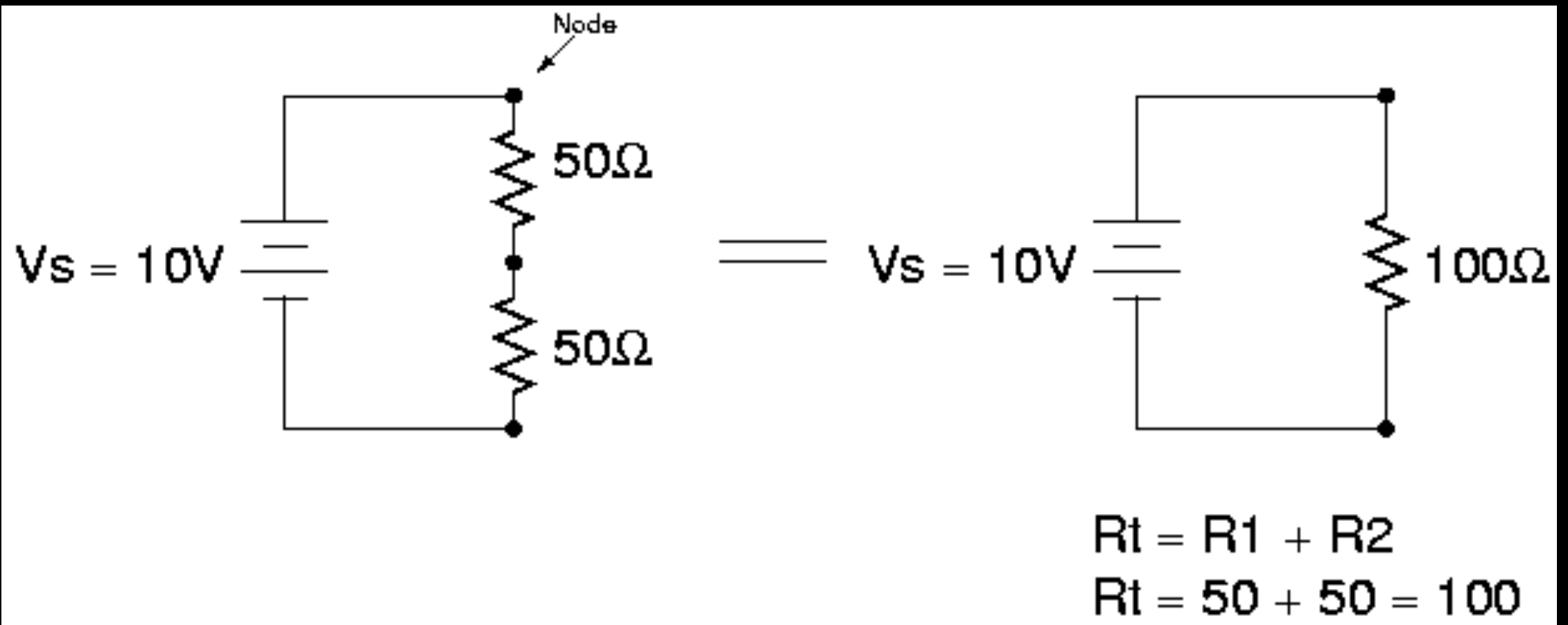

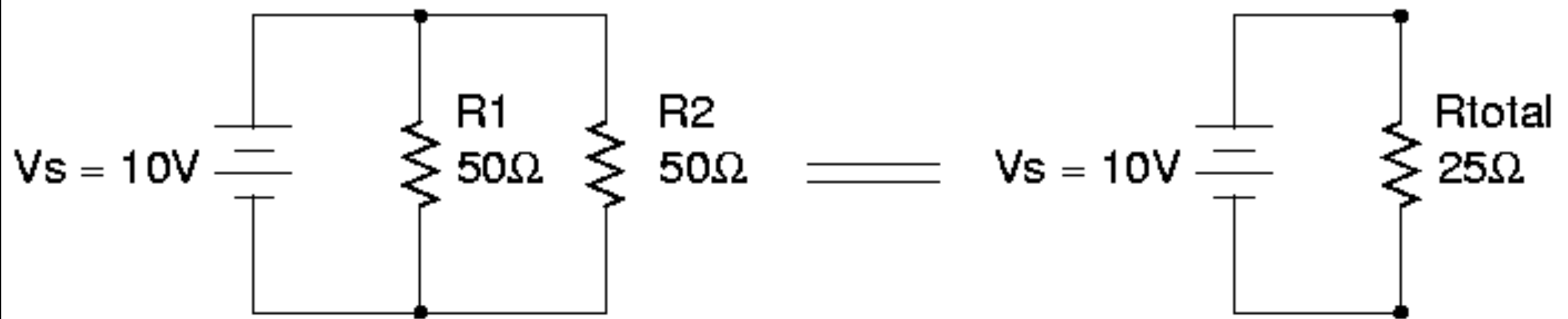

For Parallel Circuits:

$$R_{total} = (R_1 * R_2) / (R_1 + R_2)$$

