

# Displays & More

Press Play: Interactive Device Design | July 07, 2011


# Homework Sharing

Discuss Schematics with Your Neighbor(s)

Describe/Show Your Re-Purposed Products


# Interacting With Interactive Devices

## Some Sketches

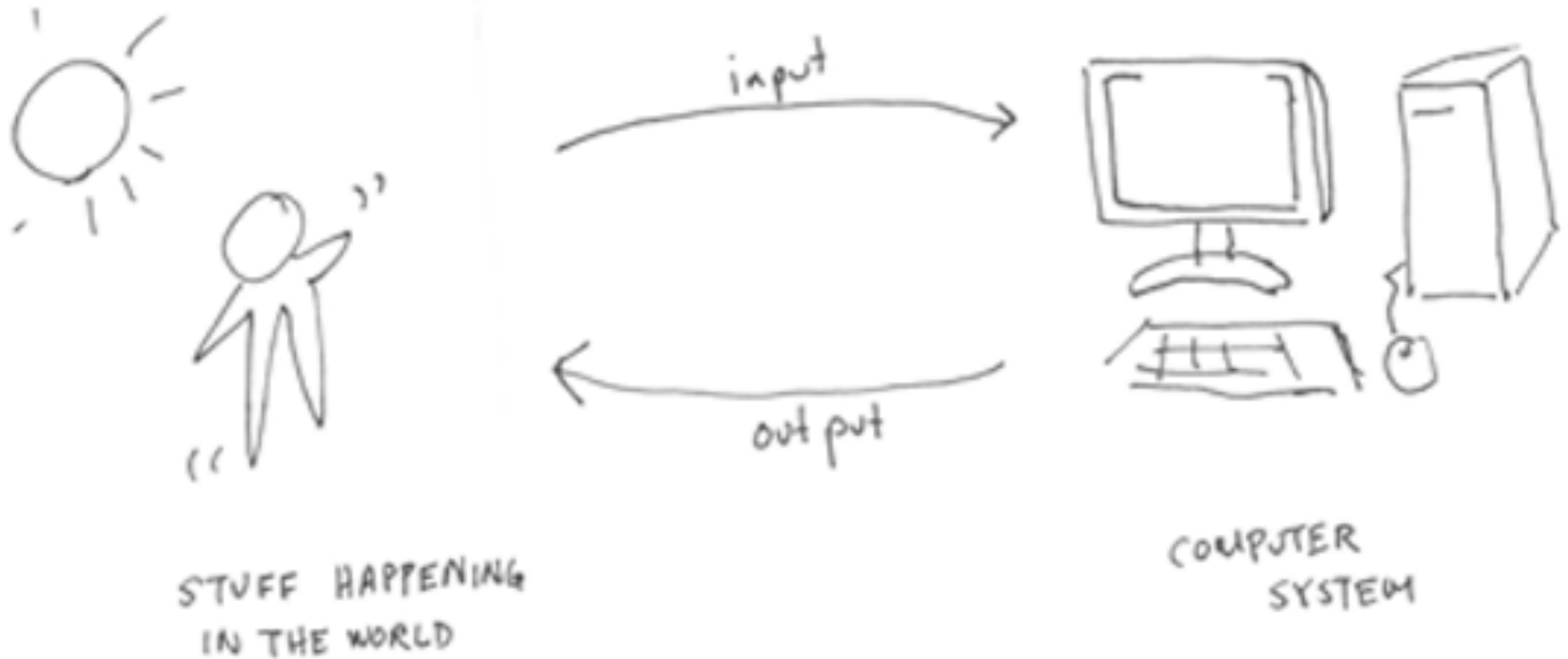


# Interacting With Interactive Devices

## Some Sketches

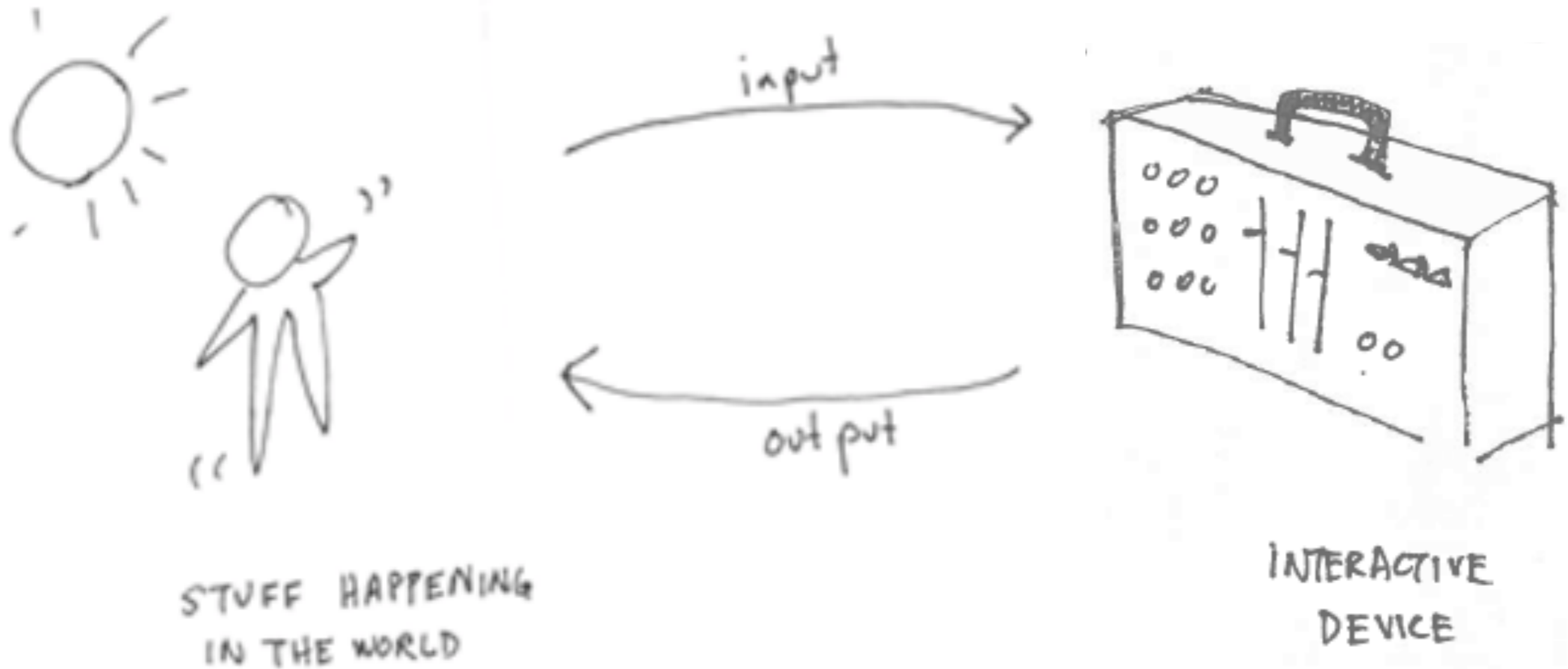


# Interacting With Interactive Devices

## Some Sketches

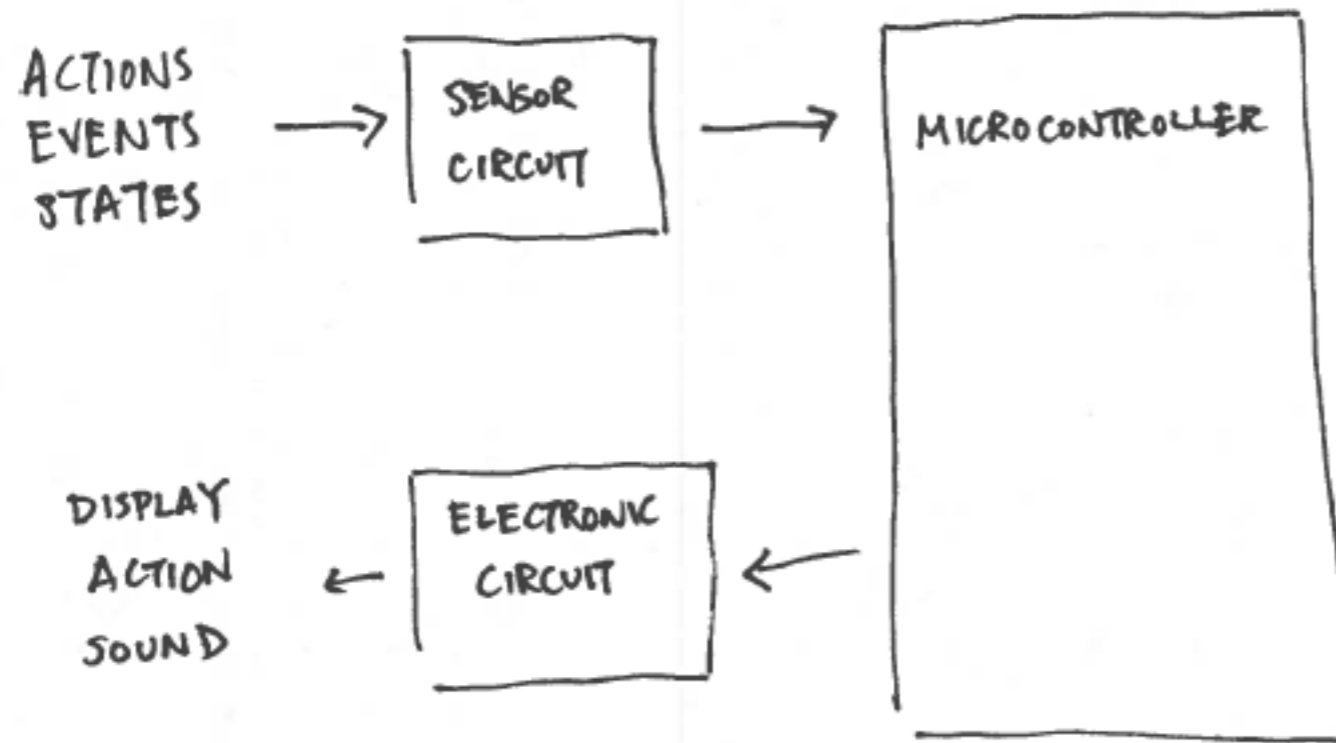


# Interacting With Interactive Devices

## Some Sketches

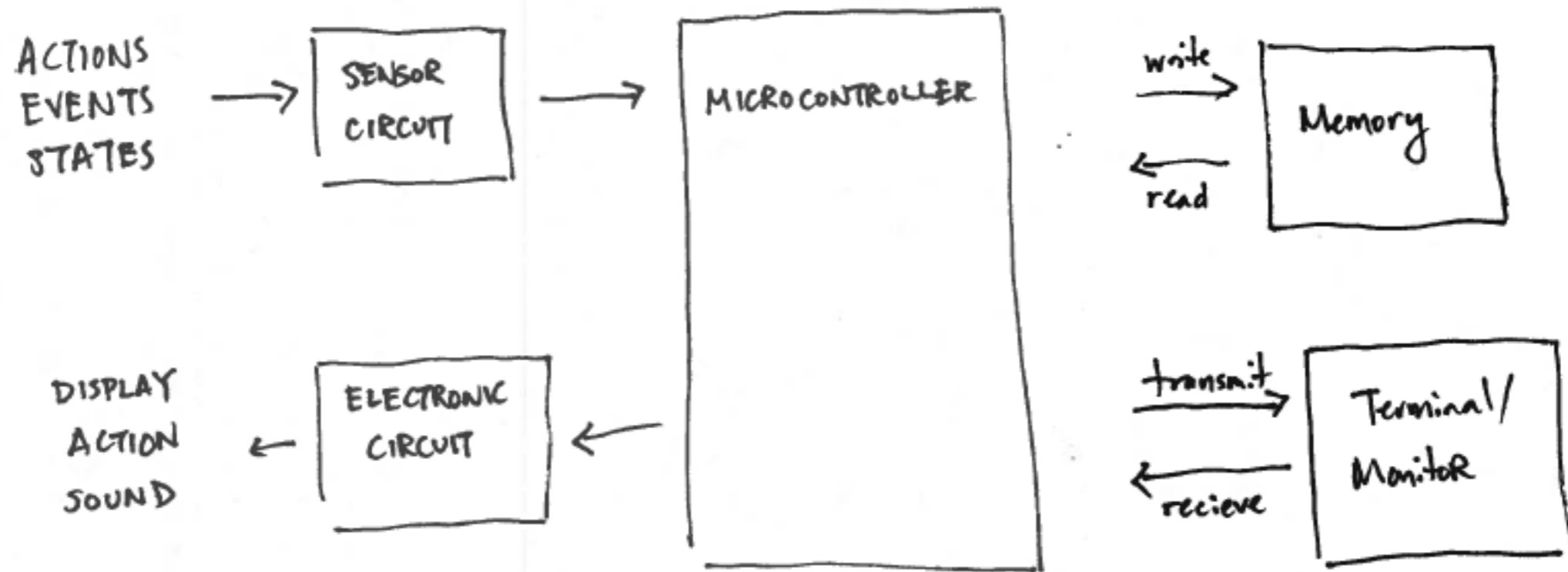



# Displays

## Variations on LEDs

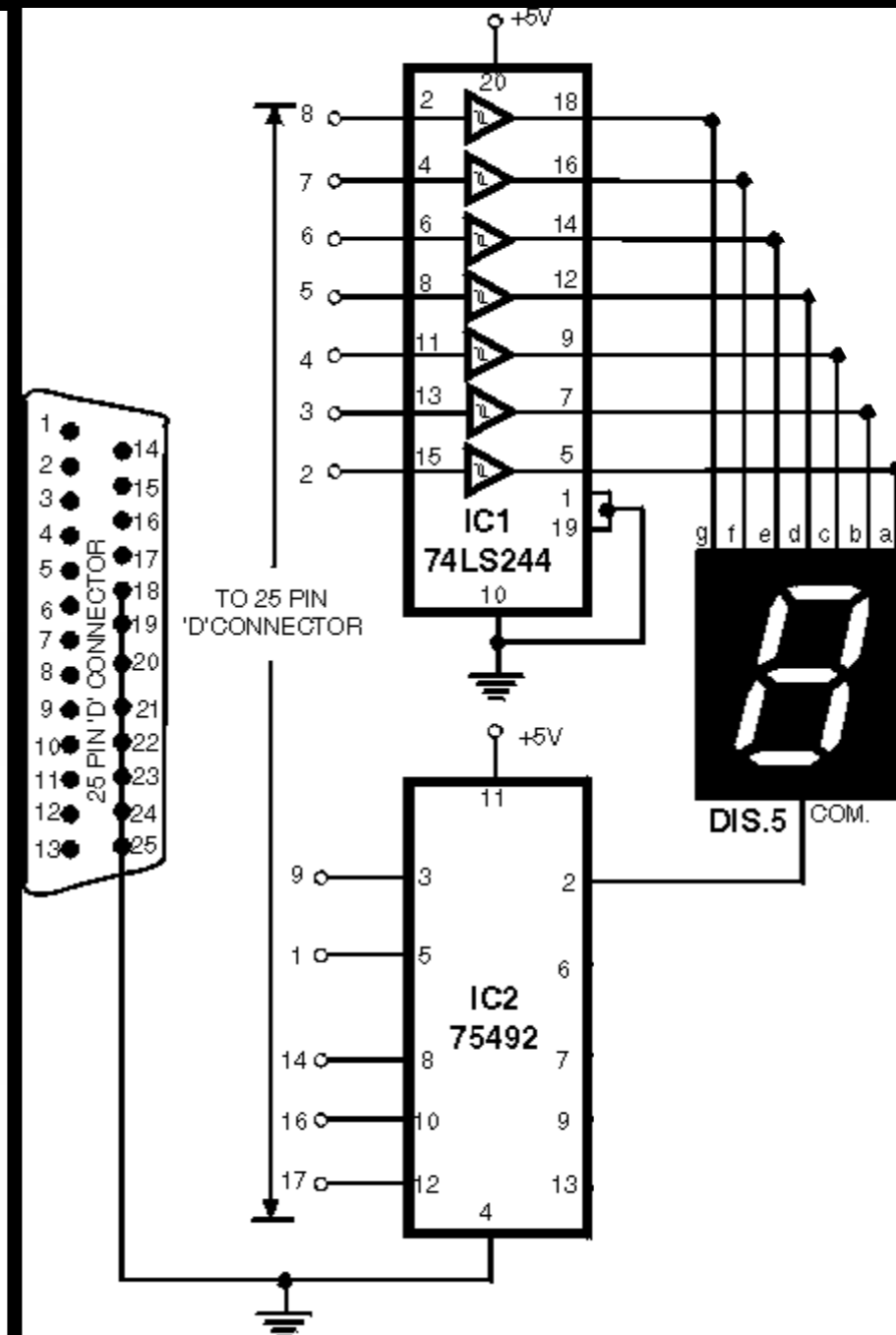

# Multiplexing



## How Does It Work?

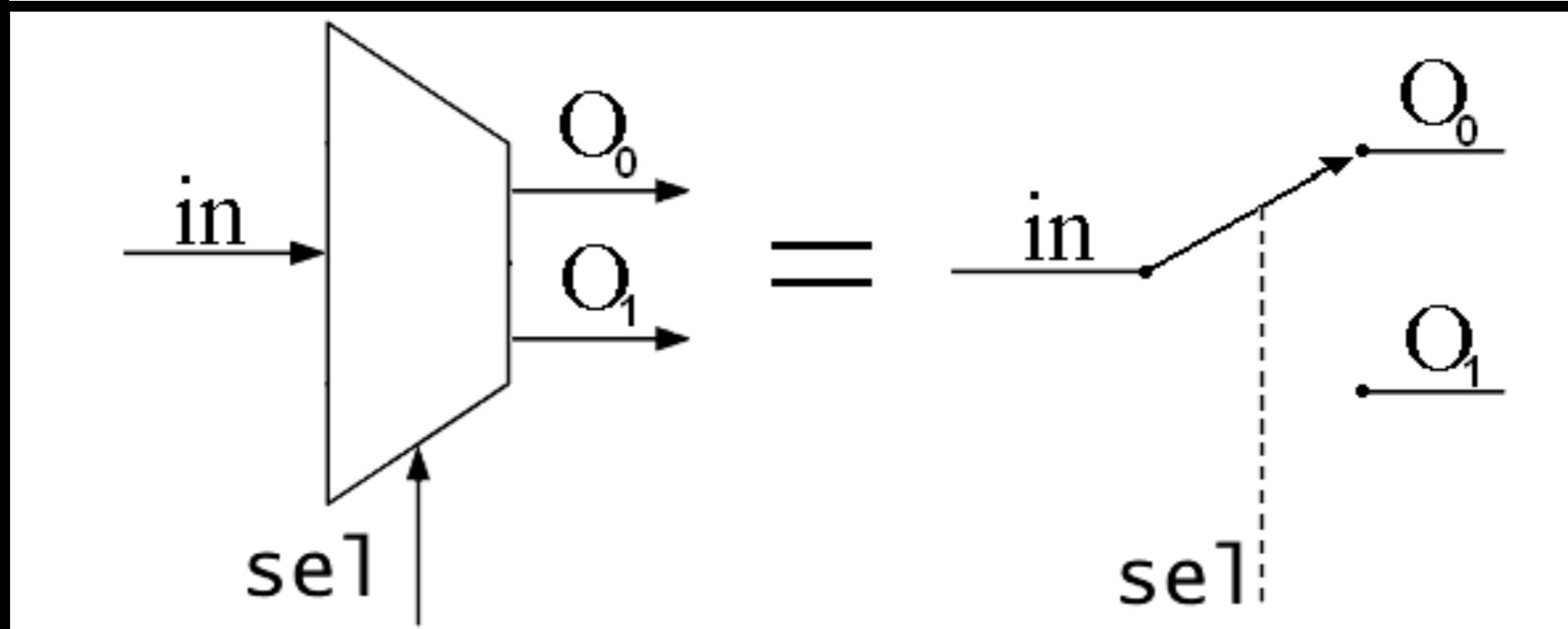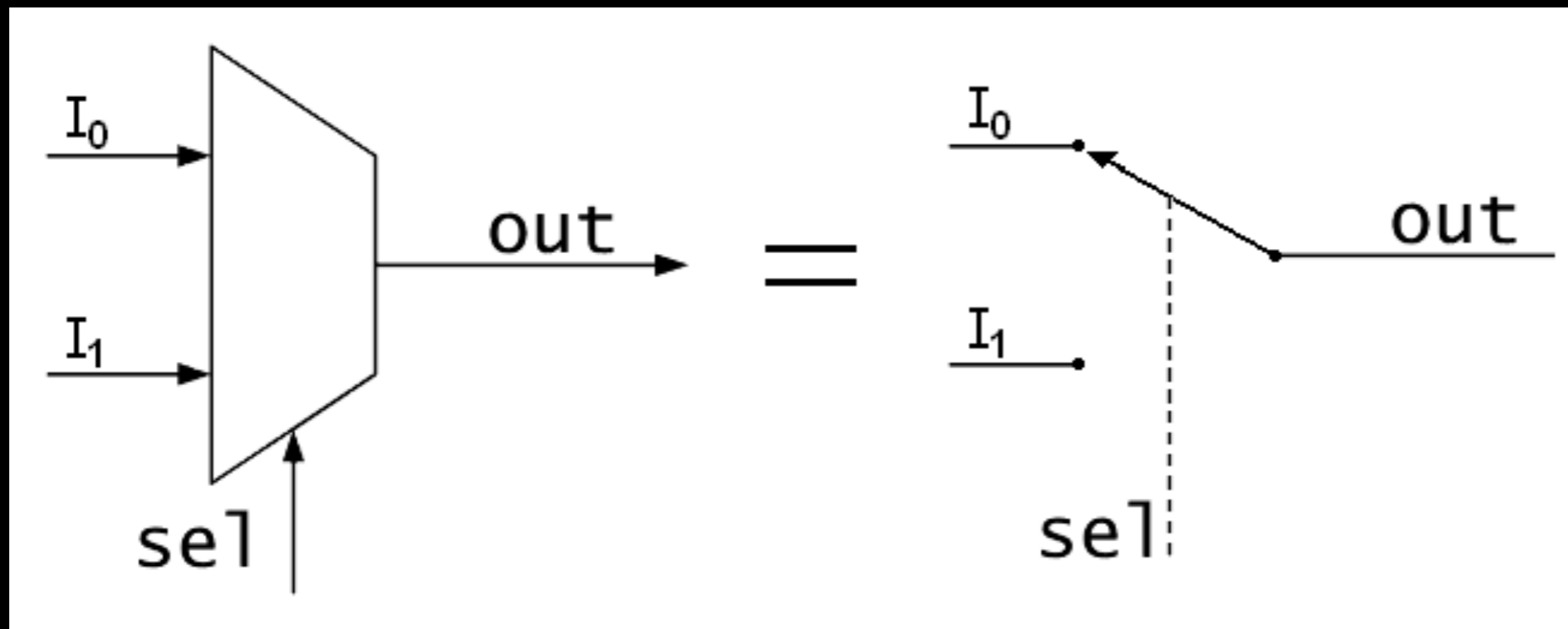





# Displays

## Variations on LEDs

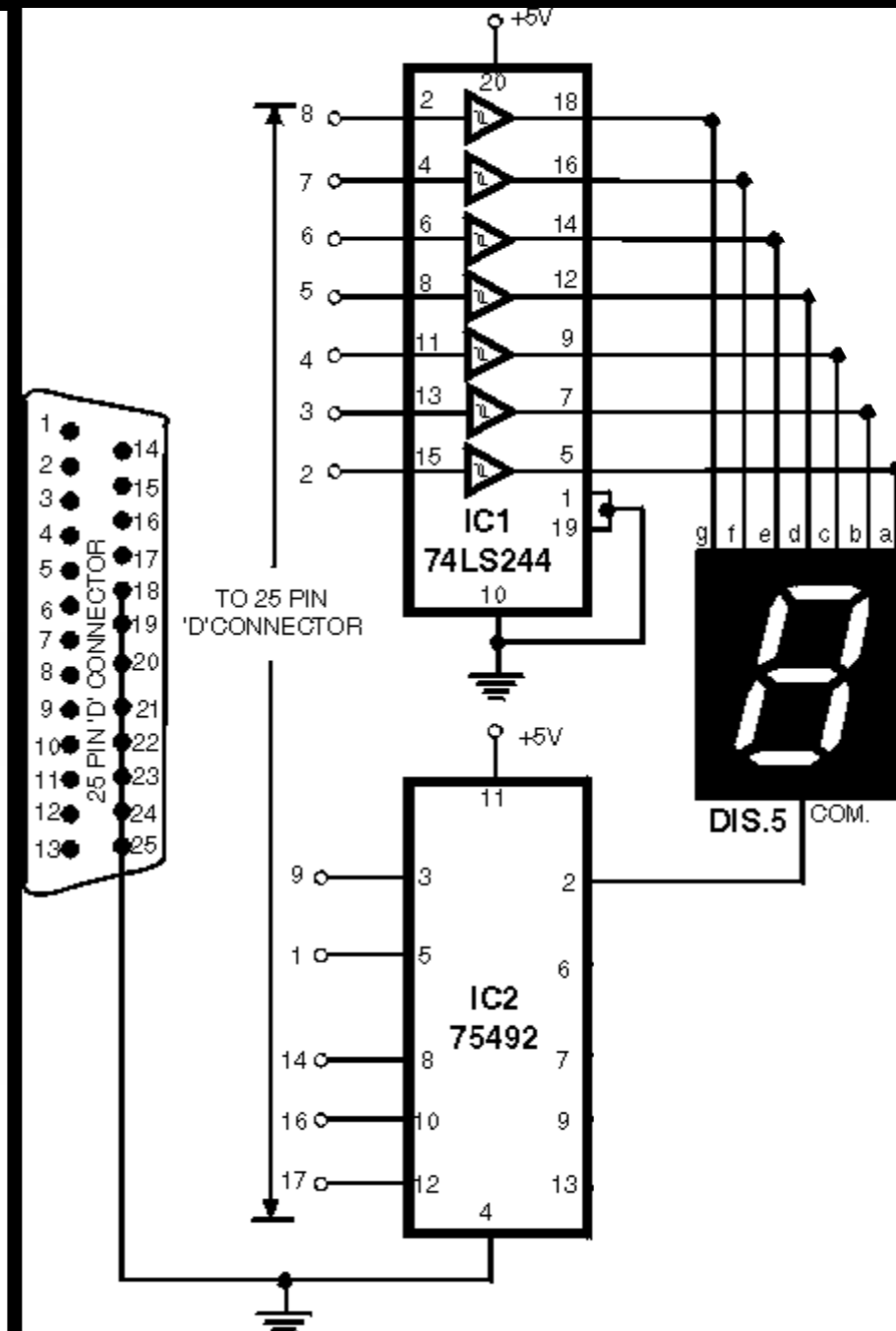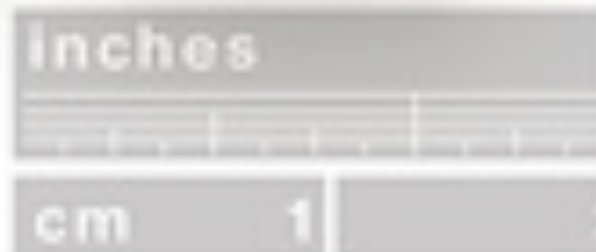


# Displays

## Variations on LEDs

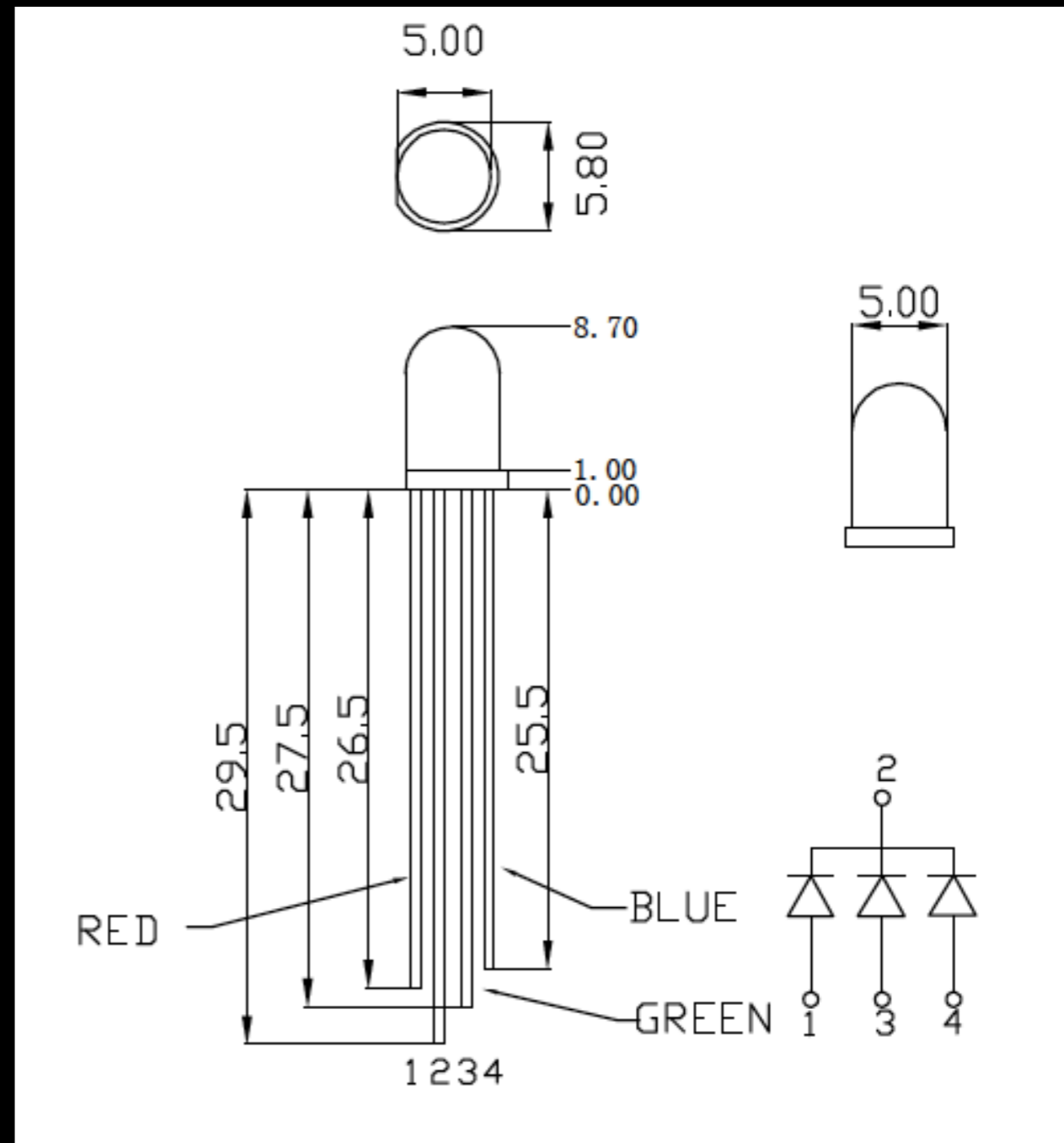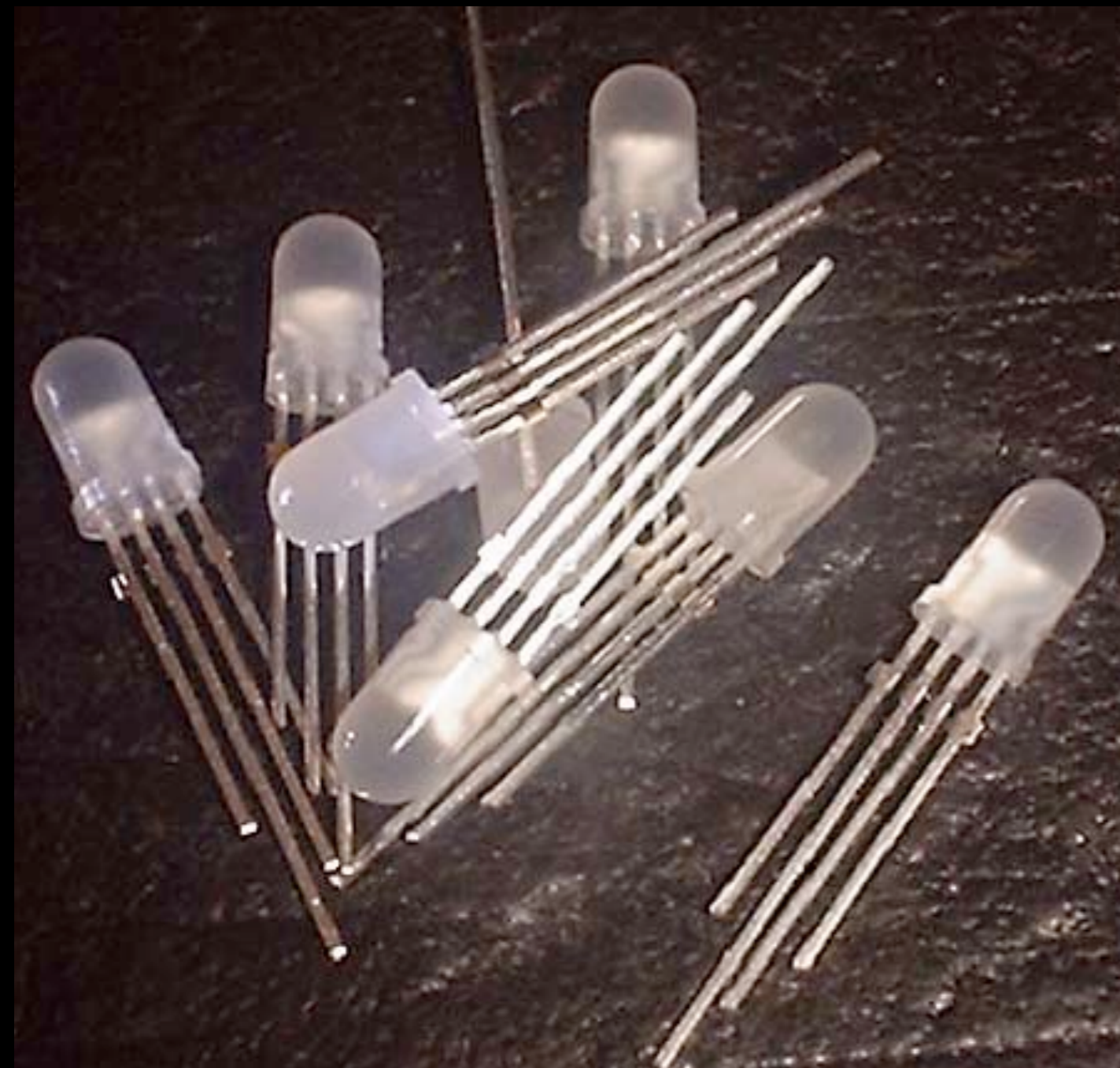

# Displays

## Variations on LEDs

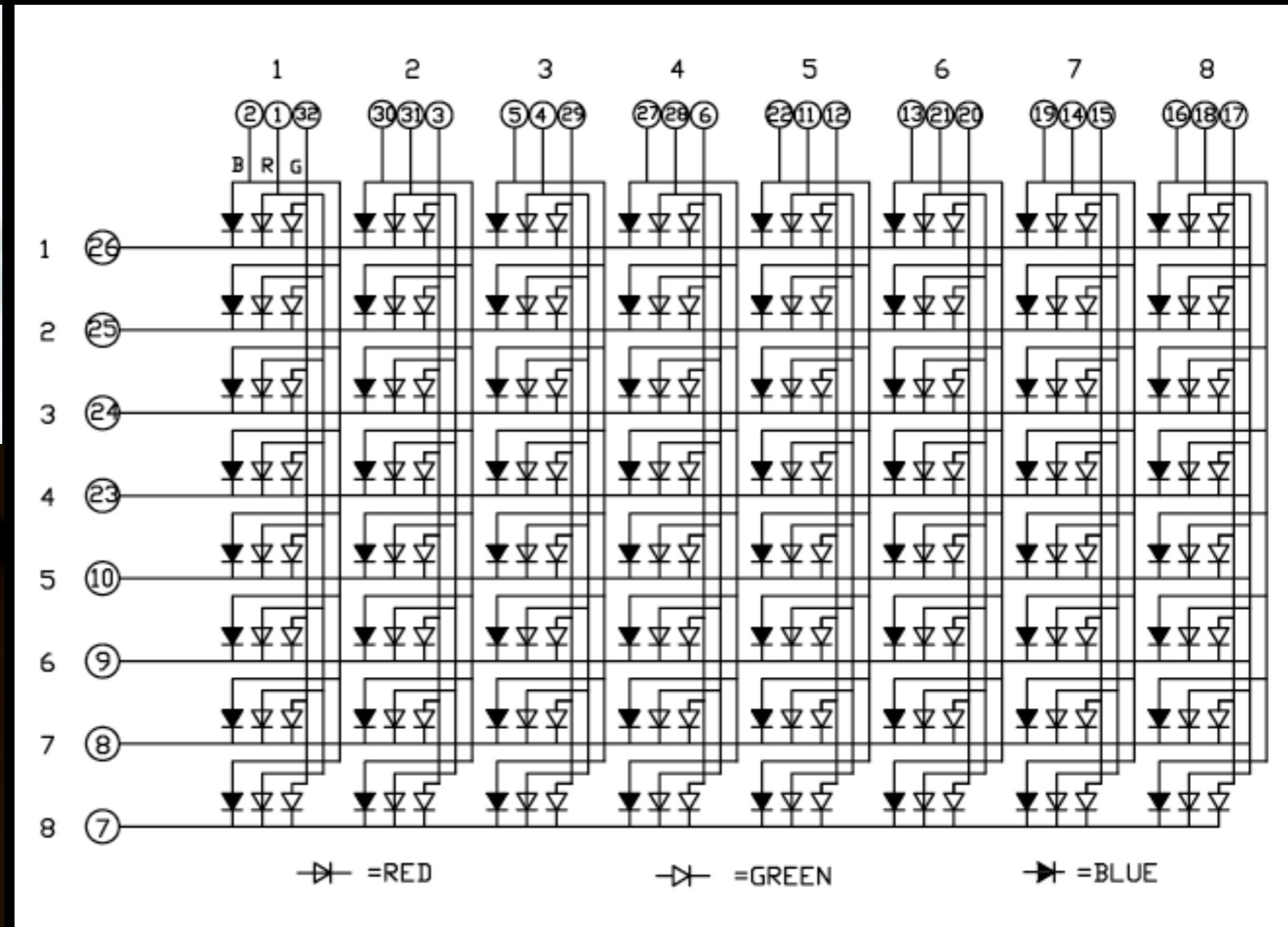

# Displays

## Character Displays



### Variations:


- Dimensions
- # Columns & Rows
- Colors
- Voltages
- Backlight
- HD44780 Compatible
- Control Interfaces  
(Parallel vs. Serial)

# Displays

## Graphical Displays
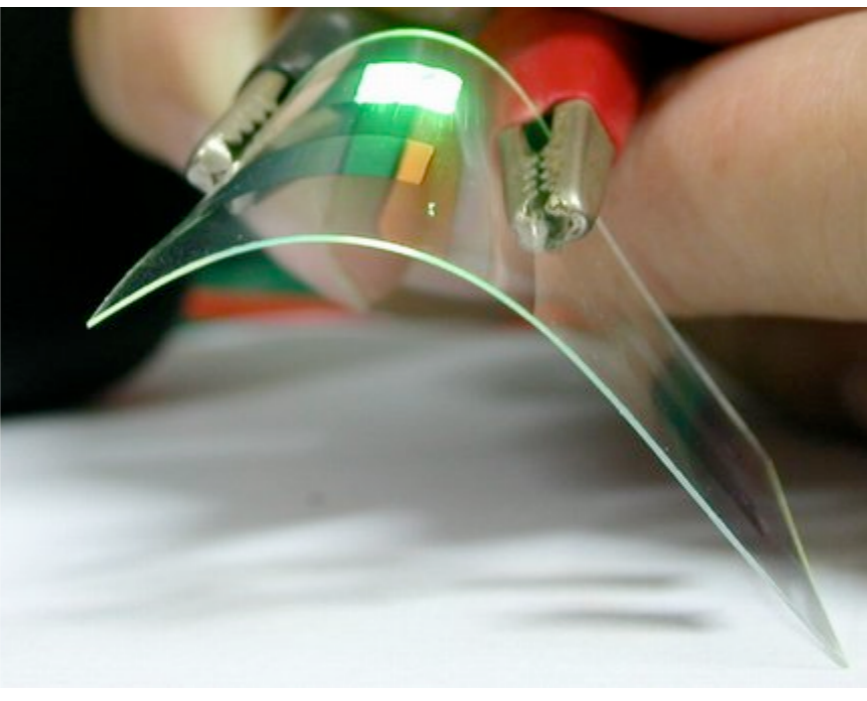
### Variations:


- Dimensions
- Pixel Width & Height
- LCD vs. OLED
- Voltages
- Backlight
- Color
- Control Interfaces



# Voltage Regulation
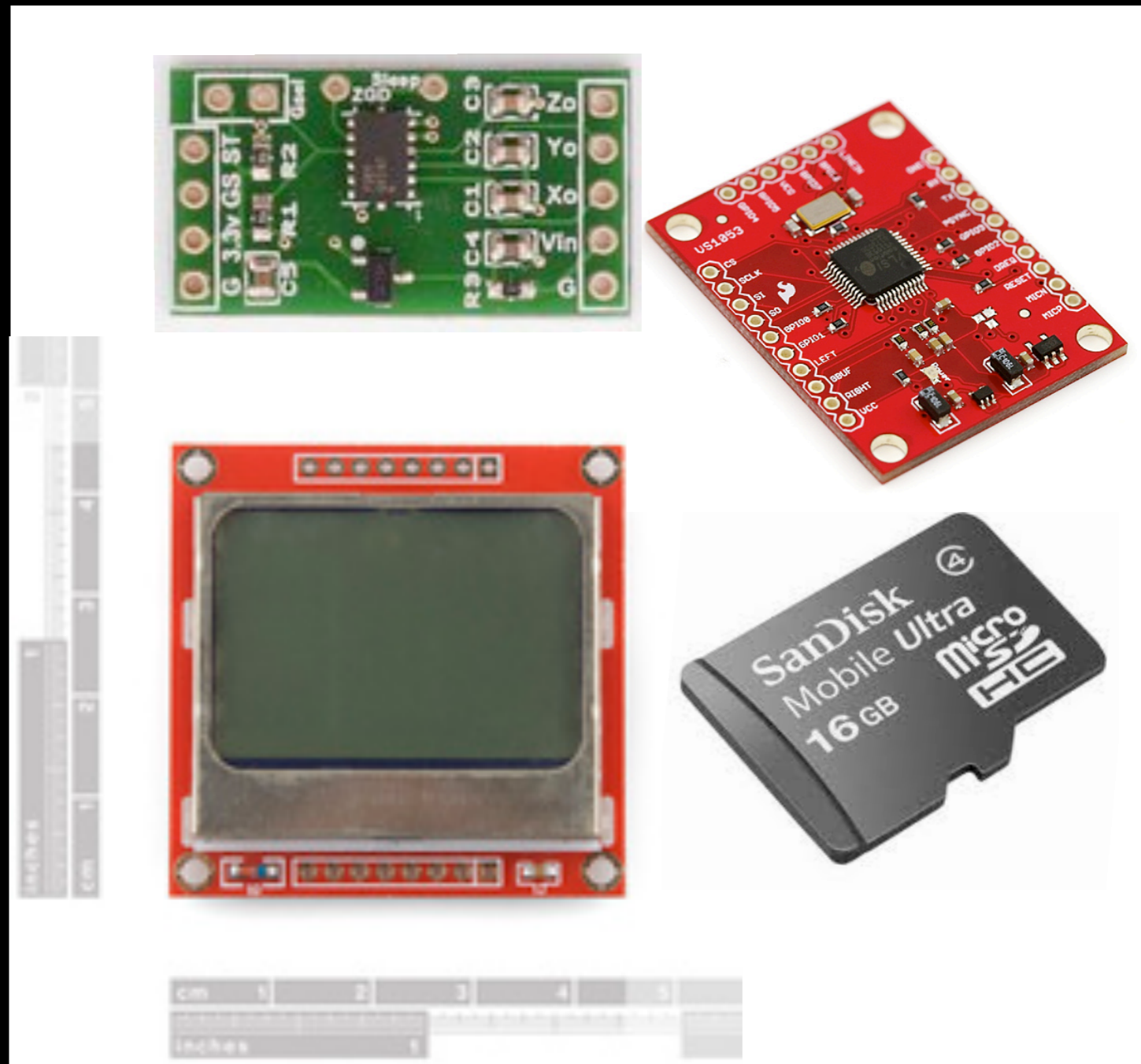
## Why Would We Want to Regulate Voltage?

The 3-Axis Accelerometer sensor will operate between 2.2 and 6 Volts. Because the MMA7361 chip only will deal with 3.6V maximum, the sensor is equipped with a low-dropout regulator so the sensor will work, out of the box, with an Arduino or other 5V microcontroller. At 5V the sensor draws around 50  $\mu$ A with the shunt off and 100  $\mu$ A with the shunt on. The current draw at 3.3V is 150 / 200  $\mu$ A respectively.




# Voltage Regulation

## How to Get the Voltage You Want

Check:

- ❑ Input/Output Voltages (LDO)
- ❑ Current Rating
- ❑ Package
- ❑ Classic 7805 Linear Regulator

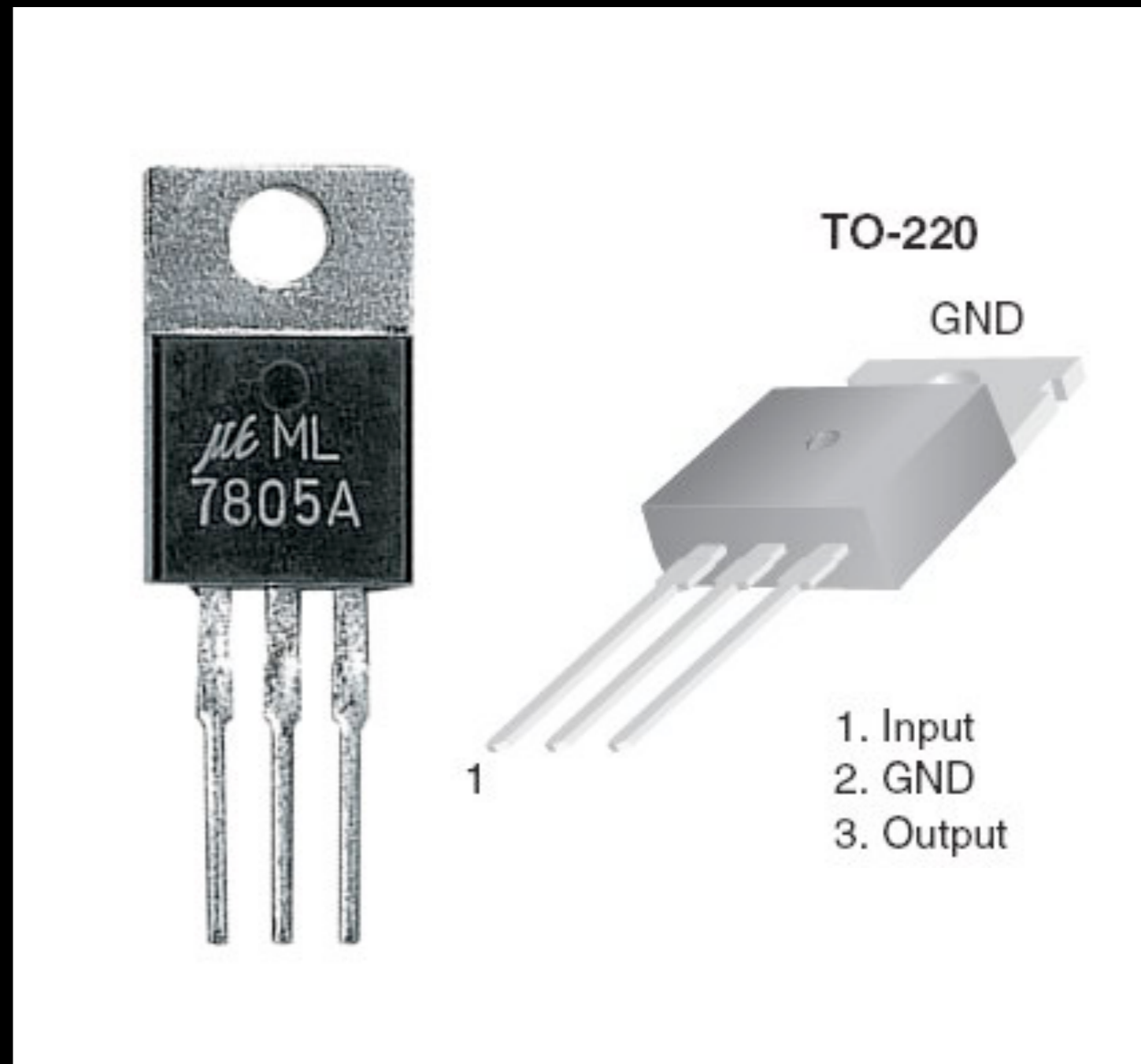The regulating device is made to act like a variable resistor, continuously adjusting a voltage divider network to maintain a constant output.



# Voltage Regulation

## How to Get the Voltage You Want

KIA7805AP/API

ELECTRICAL CHARACTERISTICS ( $V_{IN}=10V$ ,  $I_{OUT}=500mA$ ,  $0^{\circ}C \leq T_j \leq 125^{\circ}C$ )

CHARACTERISTIC	SYMBOL	TEST CIRCUIT	TEST CONDITION	MIN.	TYP.	MAX.	UNIT	
Output Voltage	$V_{OUT}$	1	$T_j=25^{\circ}C$ , $I_{OUT}=100mA$	4.8	5.0	5.2	V	
Input Regulation	Reg line	1	$T_j=25^{\circ}C$	$7.0V \leq V_{IN} \leq 25V$	-	3	100	mV
				$8.0V \leq V_{IN} \leq 12V$	-	1	50	
Load Regulation	Reg load	1	$T_j=25^{\circ}C$	$5mA \leq I_{OUT} \leq 1.4A$	-	15	100	mV
				$250mA \leq I_{OUT} \leq 750mA$	-	5	50	
Output Voltage	$V_{OUT}$	1	$7.0V \leq V_{IN} \leq 20V$ $5.0mA \leq I_{OUT} \leq 1.0A$ , $P_o \leq 15W$	4.75	-	5.25	V	
Quiescent Current	$I_B$	1	$T_j=25^{\circ}C$ , $I_{OUT}=5mA$	-	4.2	8.0	mA	
Quiescent Current Change	$\Delta I_B$	1	$7.0V \leq V_{IN} \leq 25V$	-	-	1.3	mA	
Output Noise Voltage	$V_{NO}$	1	$T_a=25^{\circ}C$ , $10Hz \leq f \leq 100kHz$ $I_{OUT}=50mA$	-	50	-	$\mu V_{rms}$	





# Voltage Regulation
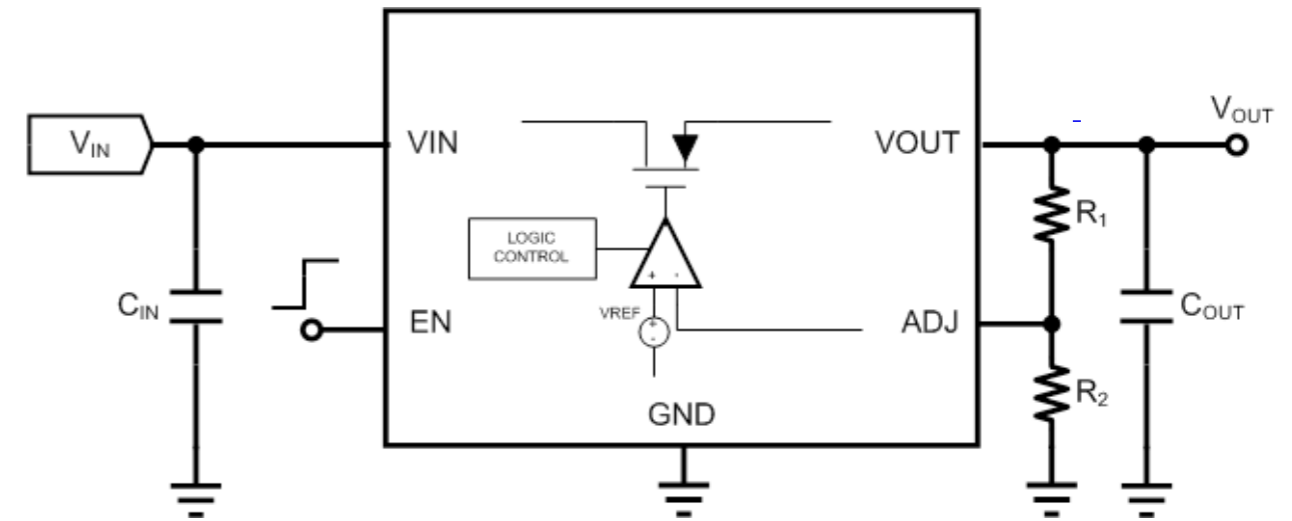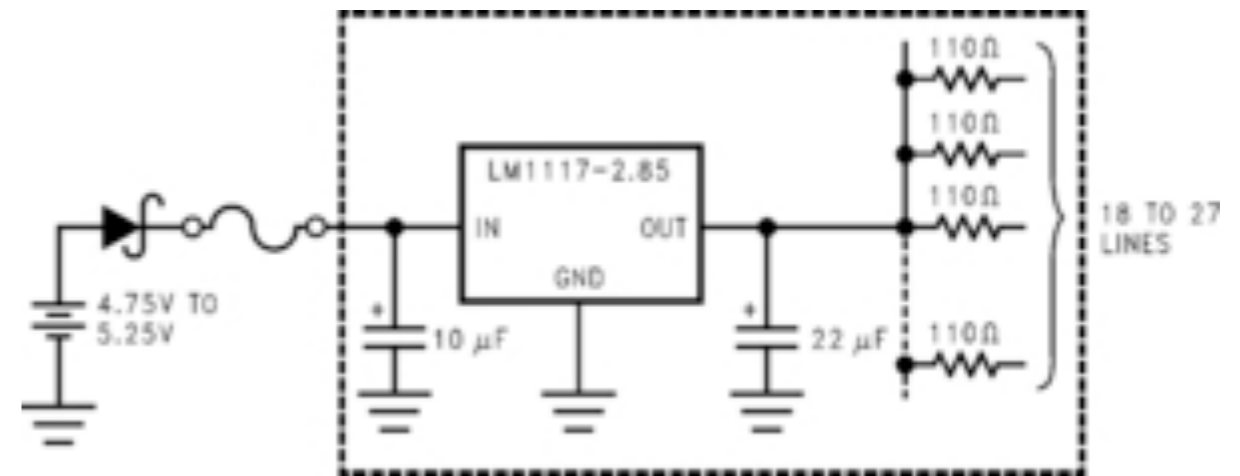
## How to Get the Voltage You Want

LM1117—3.3V 800mA  
Low Drop Out (LDO)  
Linear Regulator


Also available in 1.8V,  
2.5V, 2.85V, 3.3V, 5V  
and adjustable versions.



# Voltage Level Shifting
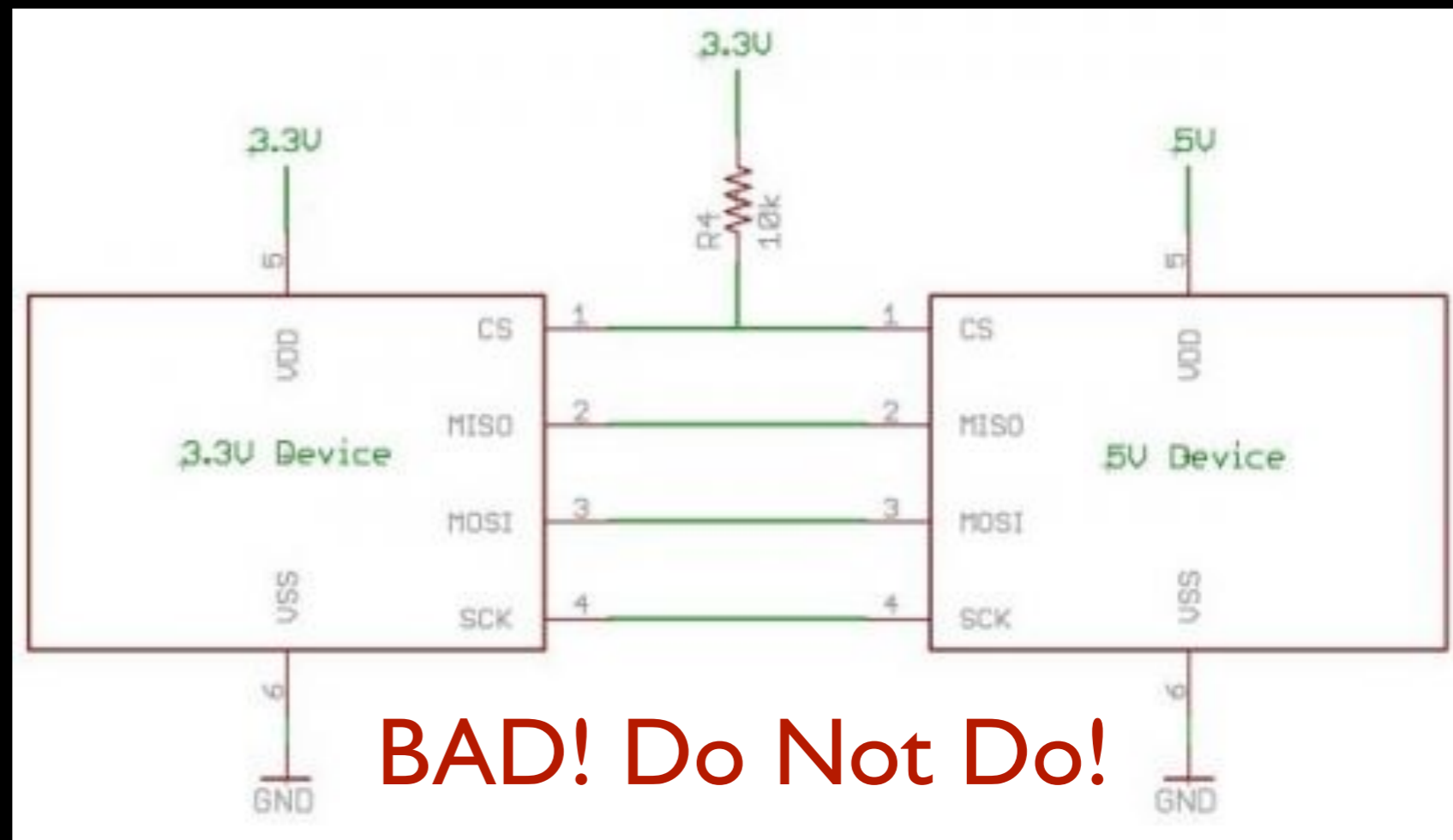
## Why Would We Want to Shift the Voltage?


- ❑ Why are there different voltages anyway?
- ❑ What can go wrong when connecting 3.3V & 5V devices?



# Voltage Level Shifting
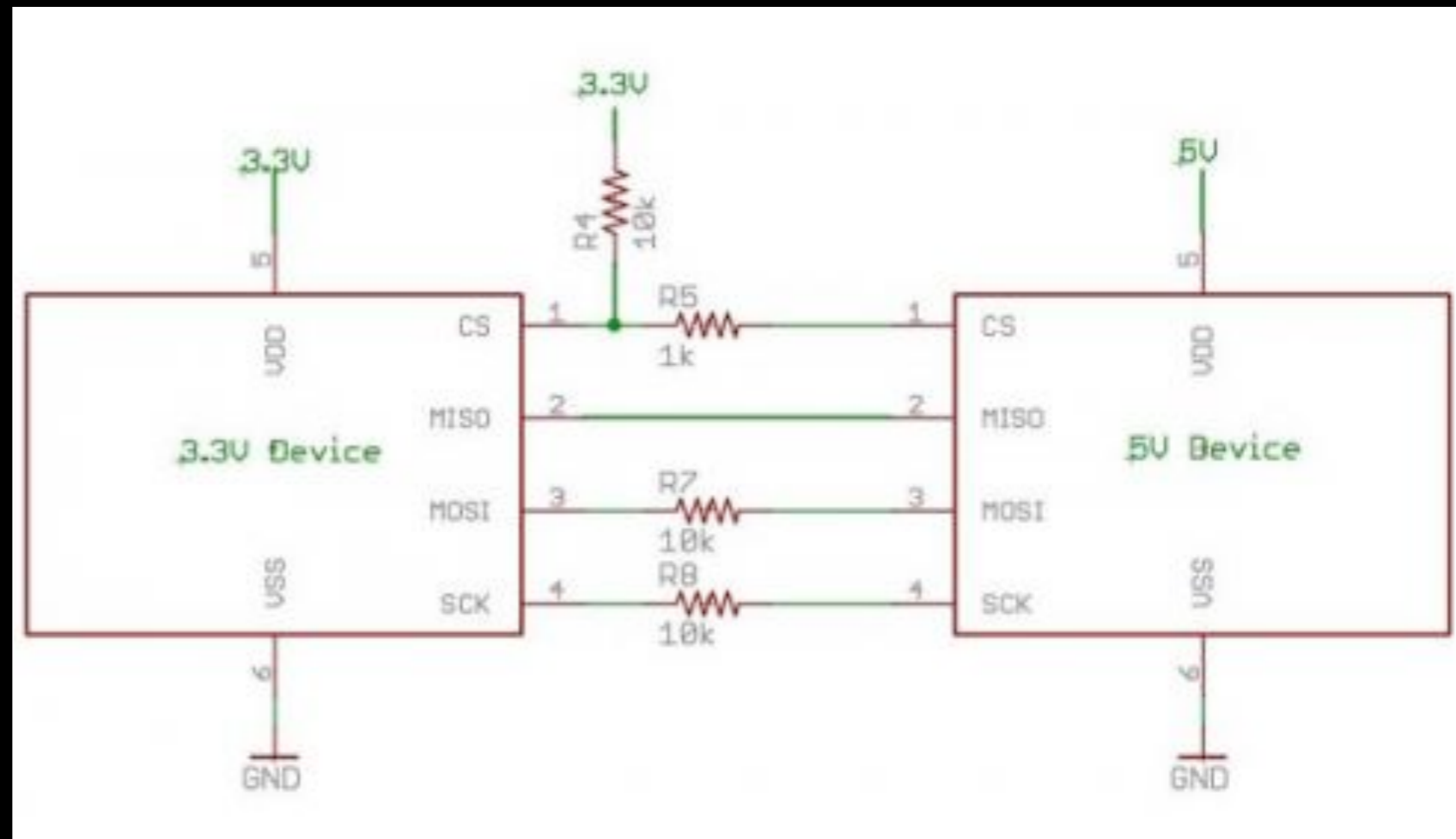
## Why Would We Want to Shift the Voltage?

- ❑ Why are there different voltages anyway?
- ❑ What can go wrong when connecting 3.3V & 5V devices?




Inline Resistor Method

# Voltage Level Shifting
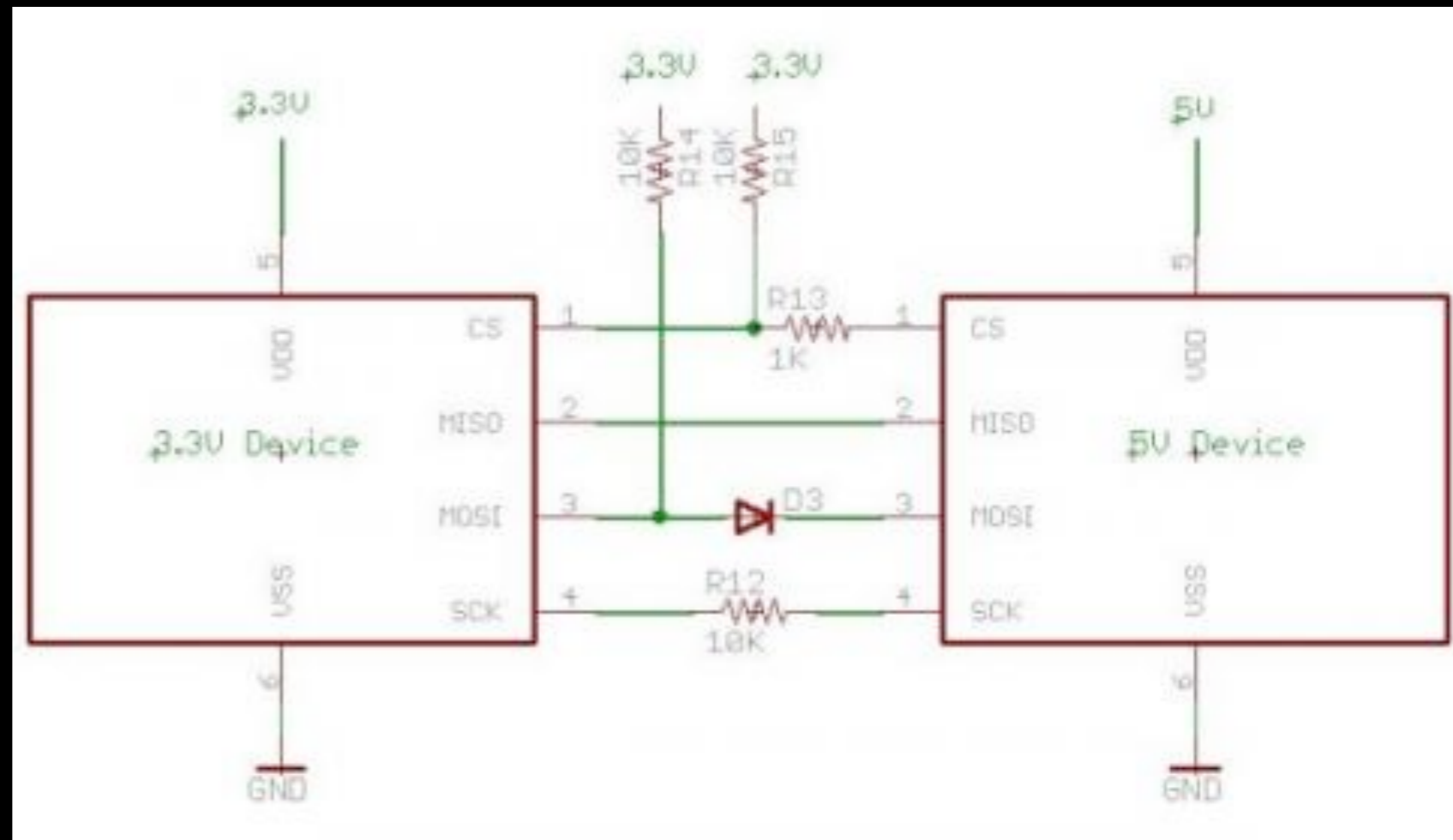
## Why Would We Want to Shift the Voltage?

- ❑ Why are there different voltages anyway?
- ❑ What can go wrong when connecting 3.3V & 5V devices?




Reverse Diode Method

# Voltage Level Shifting
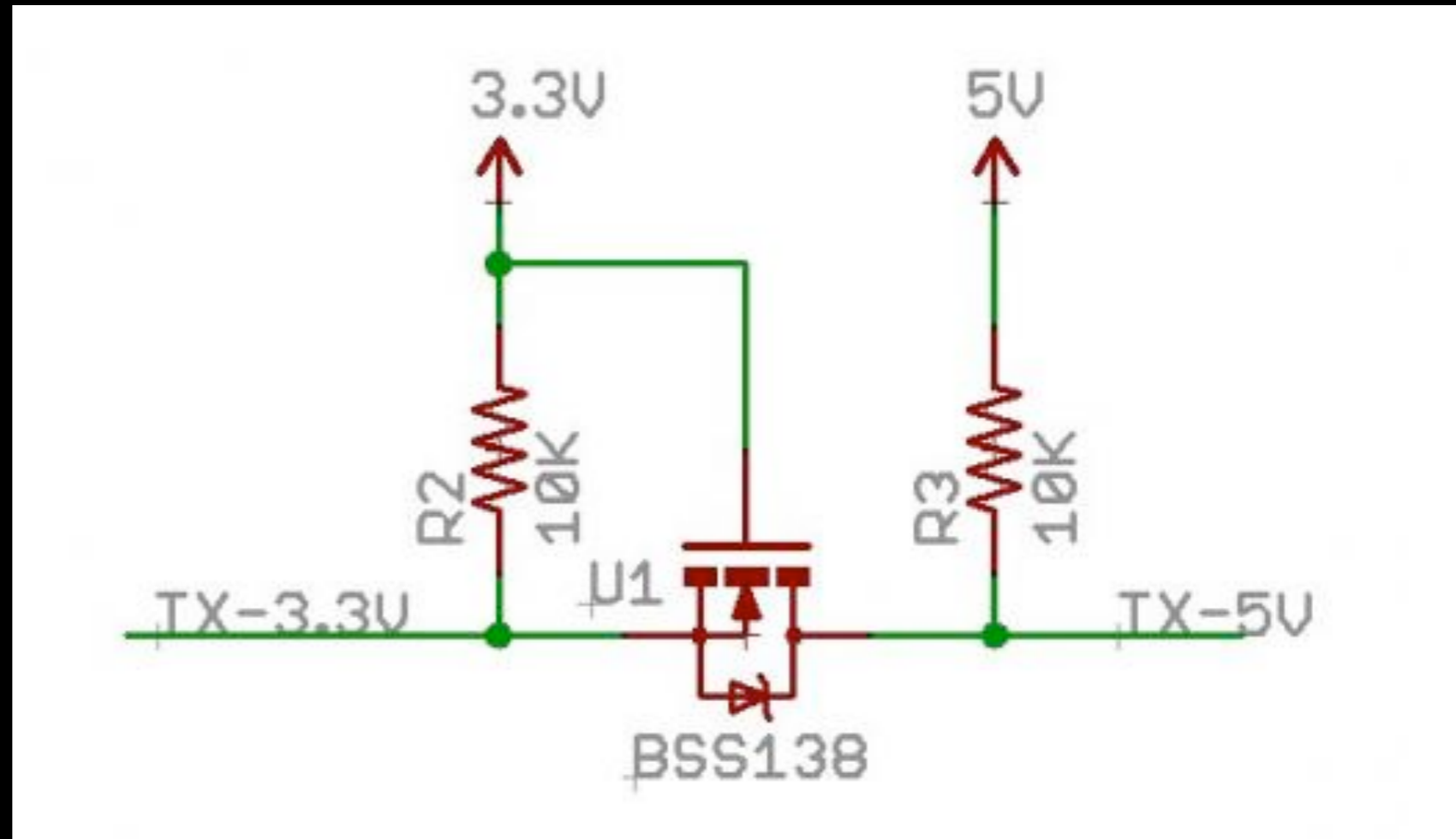
## Why Would We Want to Shift the Voltage?

- ❑ Why are there different voltages anyway?
- ❑ What can go wrong when connecting 3.3V & 5V devices?




MOSFET (Metal Oxide Semiconductor Field Effect Transistor) Method

# Voltage Level Shifting
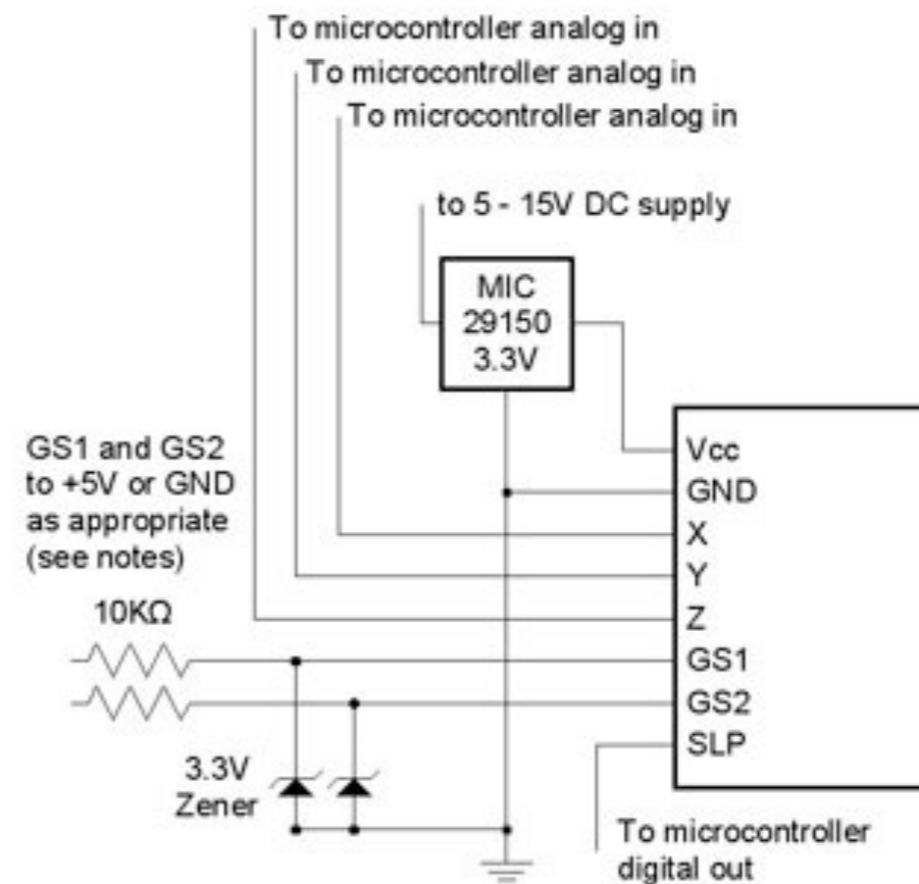
## Why Would We Want to Shift the Voltage?

- ❑ Why are there different voltages anyway?
- ❑ What can go wrong when connecting 3.3V & 5V devices?



Zener Diode Method

# Lab 4 Preview: Data Logger

Sound! Lights! Acceleration! Gesture!

Using the Serial Monitor

Writing to the EEPROM

# Homework for Next Week

5 Photos of People Listening | 2 Verplank Diagrams